

L10_1 Finite-State- Machines_Implementation

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder



Learning Objectives


- Be able to identify the components and trade-offs relevant to a finite state machine.
- Identify the course-granularity operation of the implementation for an FSM.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

FSM for Vending Machine

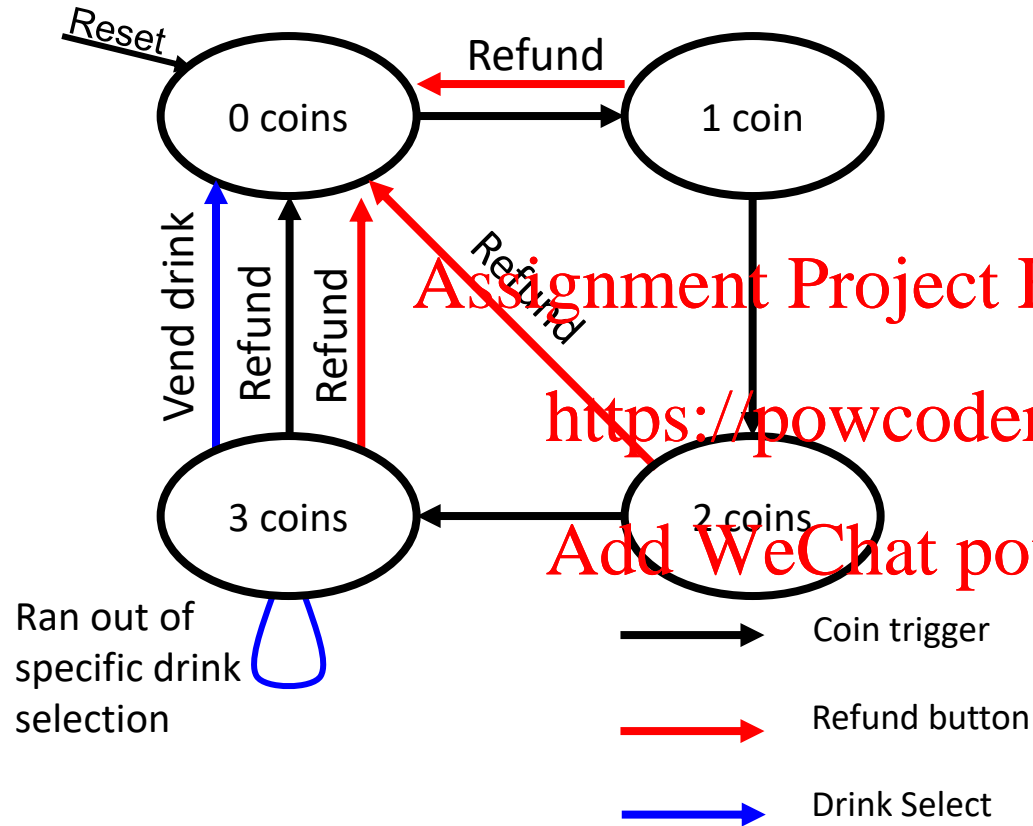

Ran out of
specific drink
selection


Is this a Mealy or Moore Machine?

Mealy ~ output is based on current state

AND input




Implementing a FSM

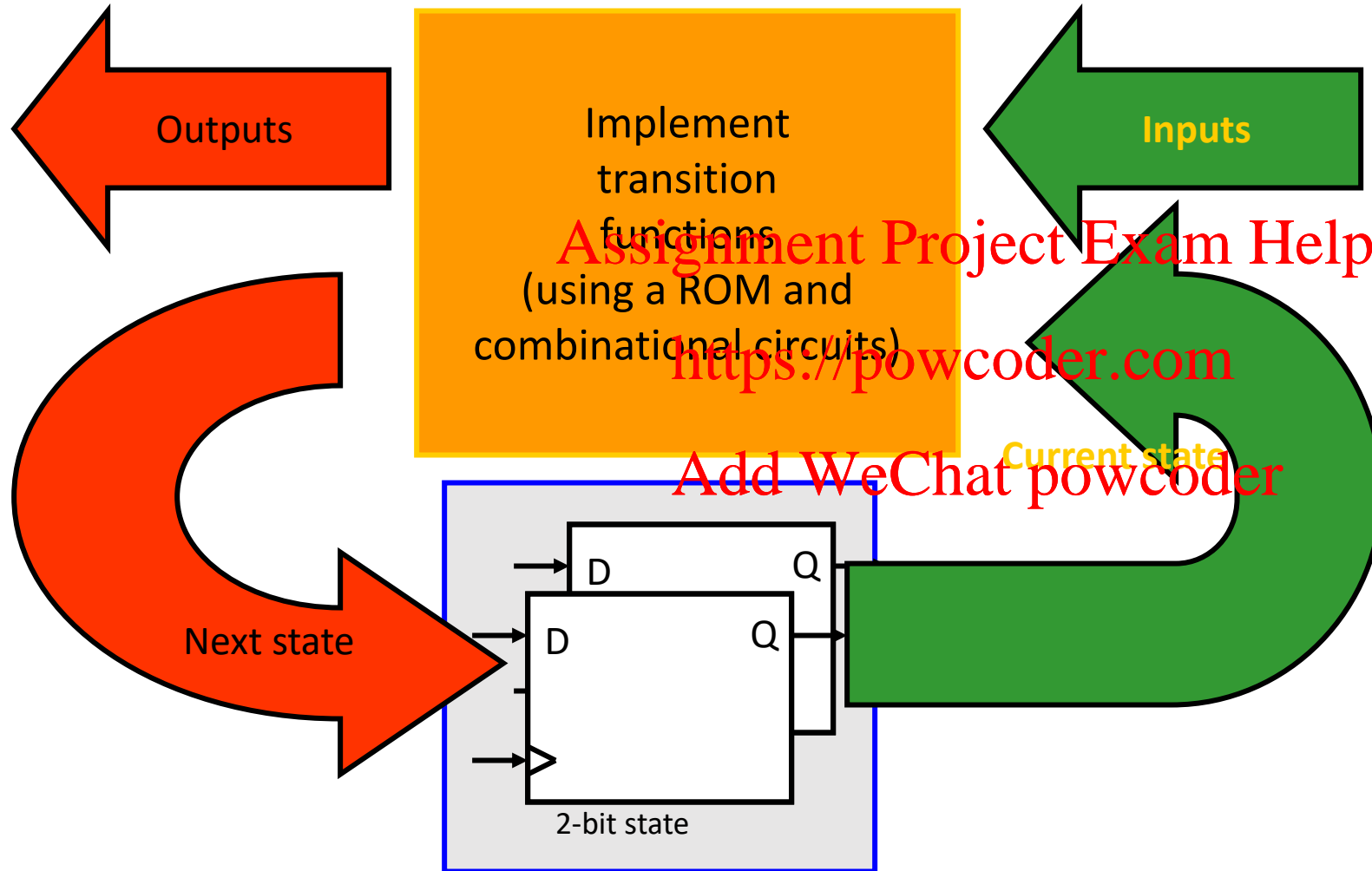

Implementing Combinational Logic (1)

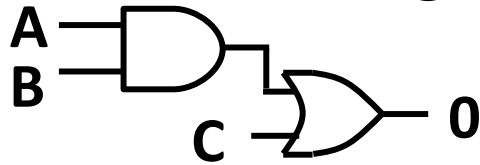- If I have a truth table:
- I can either implement this using combinational logic:




<https://powcoder.com>

Add WeChat powcoder

A	B	C	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

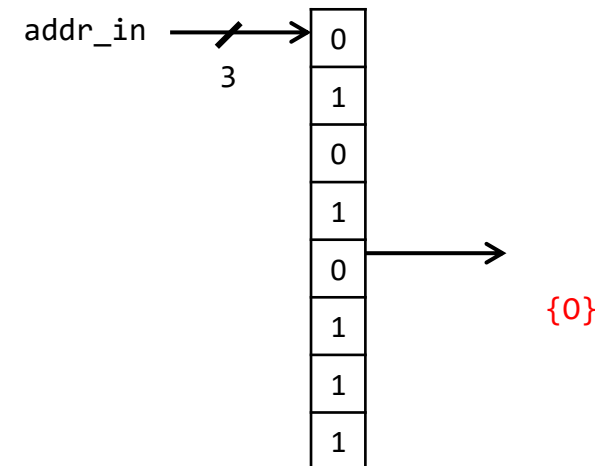- ...or I could literally just store the entire truth table in a memory and just "address" it using the input!



Implementing Combinational Logic (2)

- Custom logic

- Pros:

- Can optimize the number of gates used

- Cons:

- Can be expensive / time consuming to make custom logic circuits

- Lookup table:

- Pros:

- Programmable ROMs (Read-Only Memories) are very cheap and can be programmed very quickly

- Cons:

- Size requirement grows exponentially with number of inputs (adding one just more bit doubles the storage requirements!)

A	B	C	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Add one more input...

A	B	C	D	O
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


ROMs and PROMs

- Read Only Memory
 - Array of memory values that are constant
 - Non-volatile
- Programmable Read Only Memory
 - Array of memory values that can be written exactly once (destructive writes)
- You can use ROMs to implement FSM transition functions
 - ROM inputs (i.e., ROM address): current state, primary inputs
 - ROM outputs (i.e., ROM data): next state, primary outputs


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

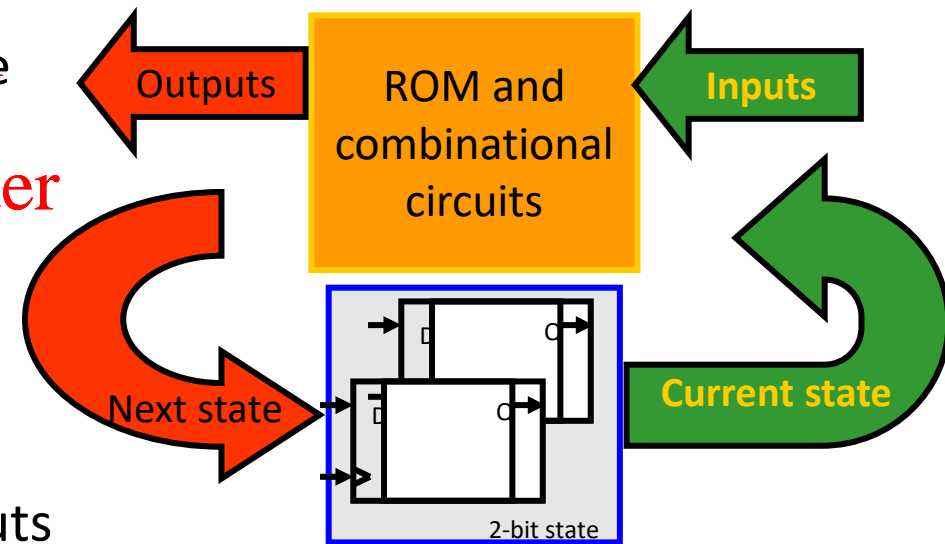

8-entry 4-bit ROM

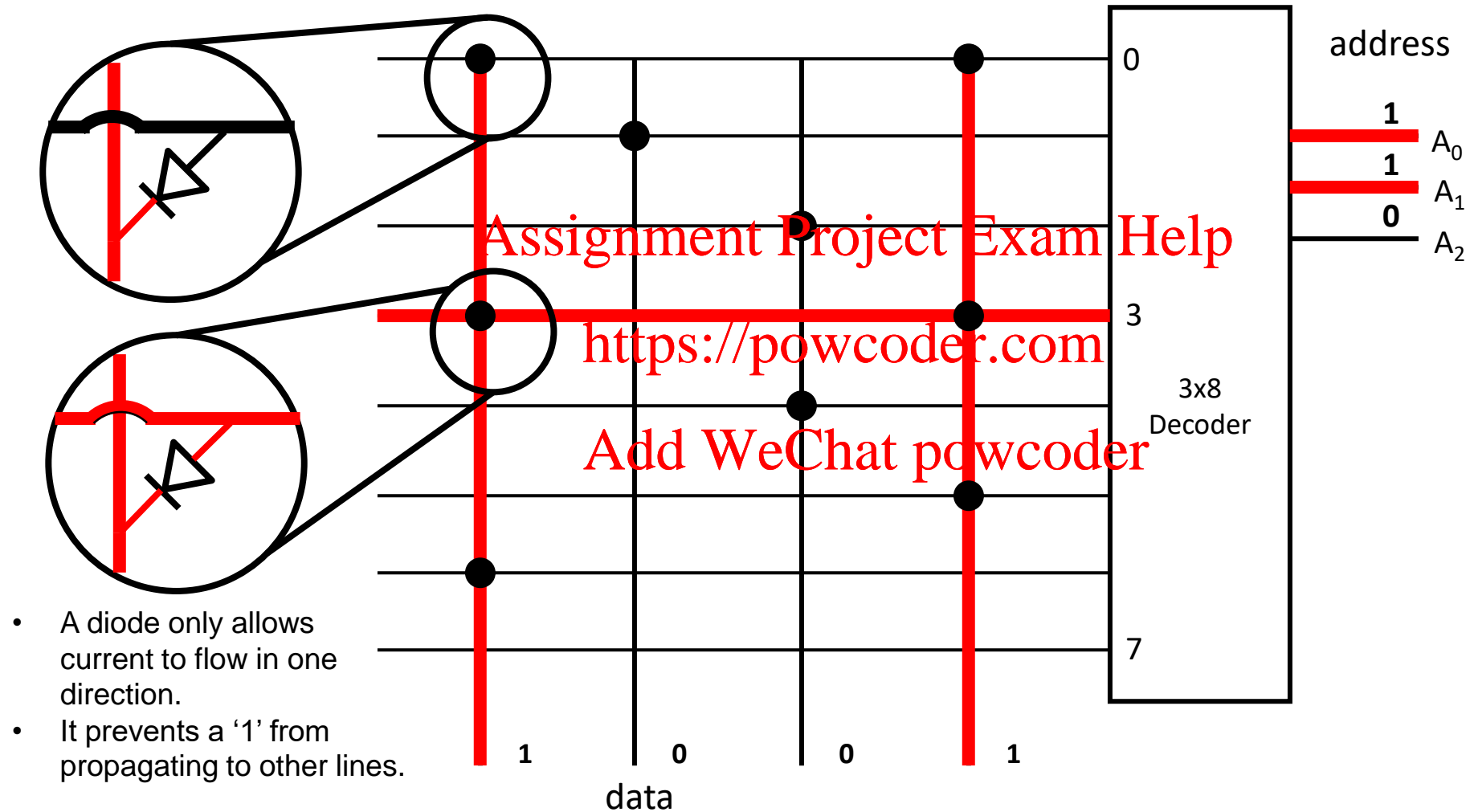

- A diode only allows current to flow in one direction.
- It prevents a '1' from propagating to other lines.

ROM for Vending Machine Controller

- Use current state and inputs as address
 - 2 state bits + 22 inputs = 24 bits (address)
 - Coin, refund, 10 drink selection, 10 sensors
- Read next state and outputs from ROM
 - 2 state bits + 11 outputs = 13 bit (memory)
 - Refund release, 10 drink latches
- We need 2^{24} entry, 13 bit ROM memories
 - 218,103,808 bits of ROM seems excessive for our cheap controller

Assignment, Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Reducing the ROM Needed


- Idea: let's do a hybrid between combinational logic and a lookup table
 - Use basic hardware (AND / OR) gates where we can, and a ROM for everything more complicated
- Replace 10 selector inputs and 10 pressure inputs with a single bit input (drink selected)
 - Use drink selection input to specify which drink release latch to activate
 - Only allow trigger if pressure sensor indicates that there is a bottle in that selection. (10 2-bit ANDs)
- Now:
 - 2 current state bits + 3 input bits (5 bit ROM address)
 - 2 next state bits + 2 control trigger bits (4 bit memory)
 - $32 \times 4 = 128$ bit ROM (good!)

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

Putting It All Together

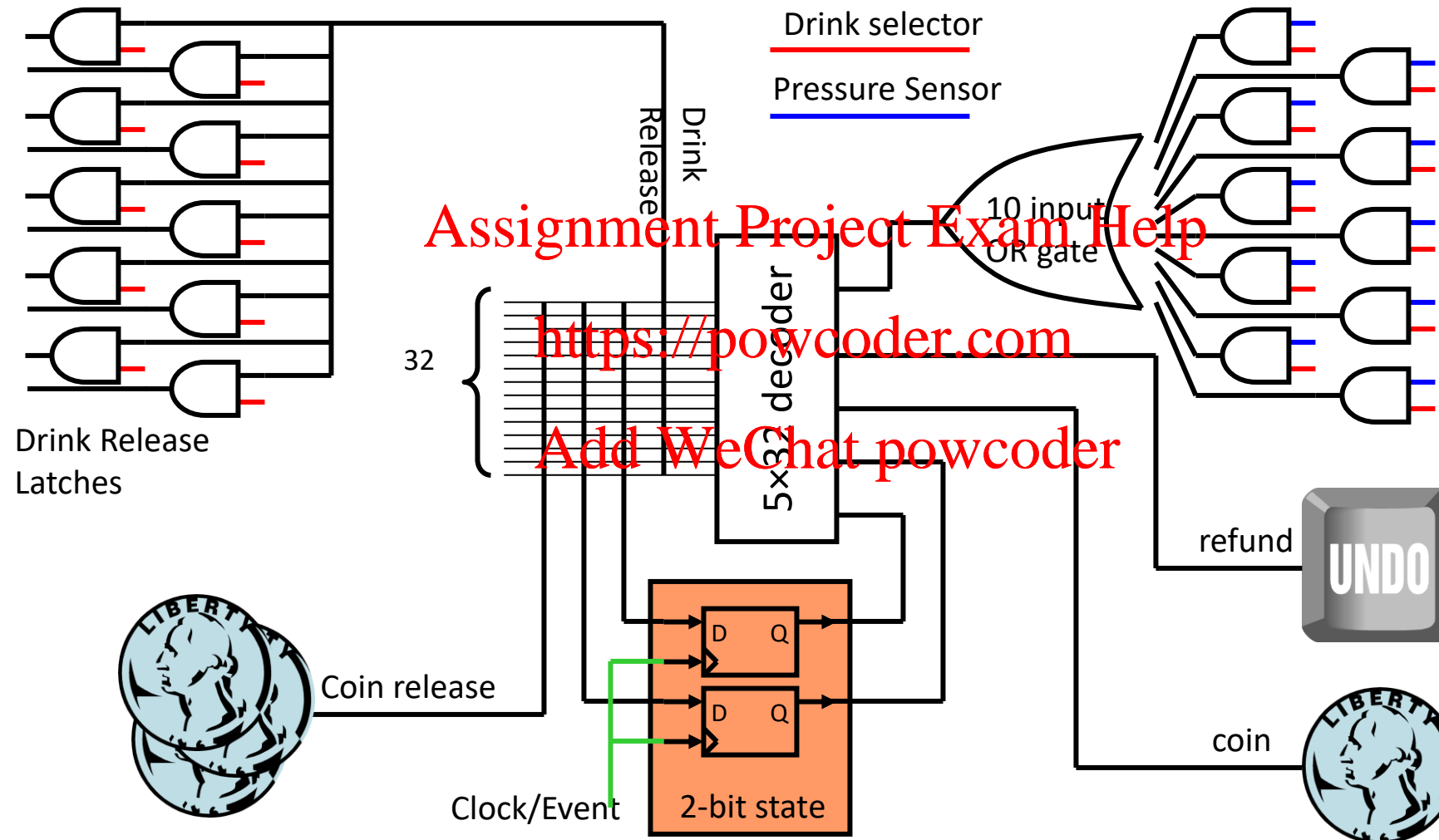

Some of the ROM Contents

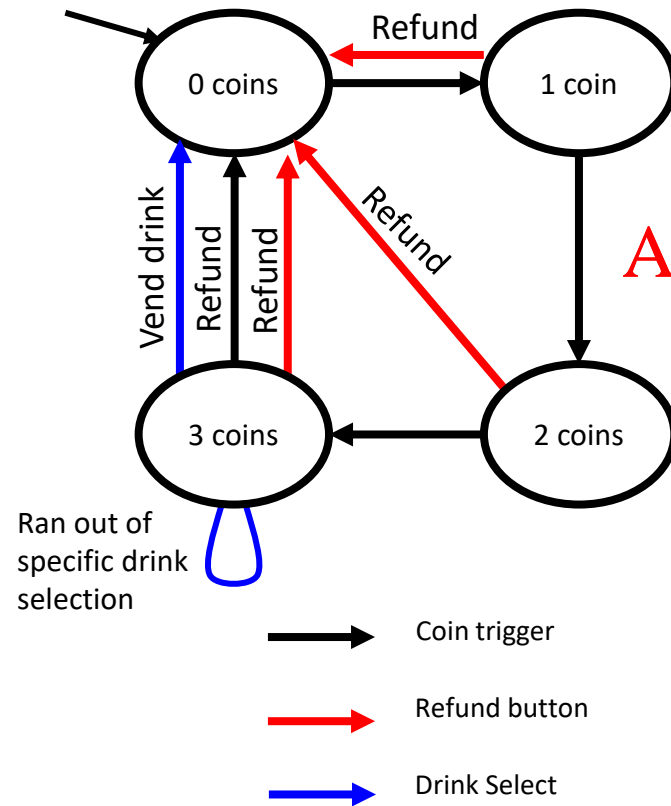

Current state	Coin trigger	Drink select	Refund button	Next state	Coin release	Drink release
0 0	0	0	0	0 0	0	0
0 0	0	0	1	0 0	0	0
0 0	1	0	0	0 1	0	0
0 1	1	0	0	1 1	0	0
1 0	1	0	0	0 0	1	0
1 1	1	0	0	0 0	1	0
... 24 more entries				... 24 more entries		

ROM address (current state, inputs)

ROM contents (next state, outputs)

Limitations of the Controller


- What happens if we make the price \$1.00?, or what if we want to accept nickels, dimes and quarters?
 - Must redesign the controller (more state, different transitions)
 - A programmable processor only needs a software upgrade.
 - If you had written software anticipating a variable price, perhaps no change is even needed
- Next Topic - Our first processor!

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

LC2Kx Processor as FSM

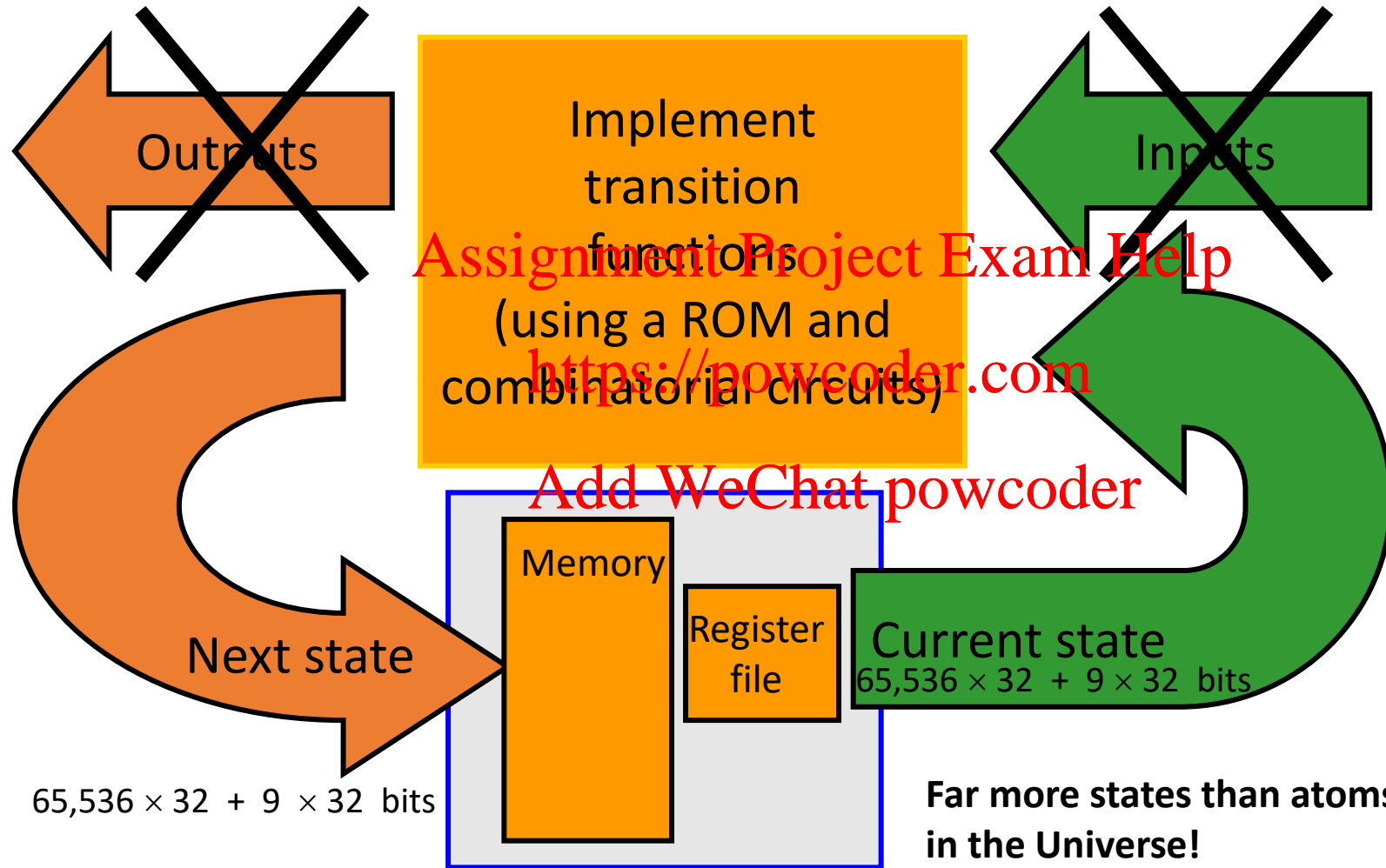


Logistics

- There are 3 videos for lecture 10
 - L10_1 – Finite-State-Machines_Implementation
 - L10_2 – Single-Cycle Processor
 - L10_3 – LC2K_Datapath
- There is one worksheet for lecture 10
 1. Finite state machine – you can do this now

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



L10_2 Single-Cycle-Processor

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder



Learning Objectives

- To identify the components used to implement a processor for LC-2K and understand the mapping from these components to LC-2K instructions.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Single-Cycle Processor Design

General-Purpose Processor Design


- Fetch Instructions
- Decode Instructions
 - Instructions are input to control ROM
- ROM data controls movement of data
 - Incrementing PC, reading registers, ALU control
- Clock drives it all
- Single-cycle datapath: Each instruction completes in one clock cycle

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

Building Blocks for the LC2K

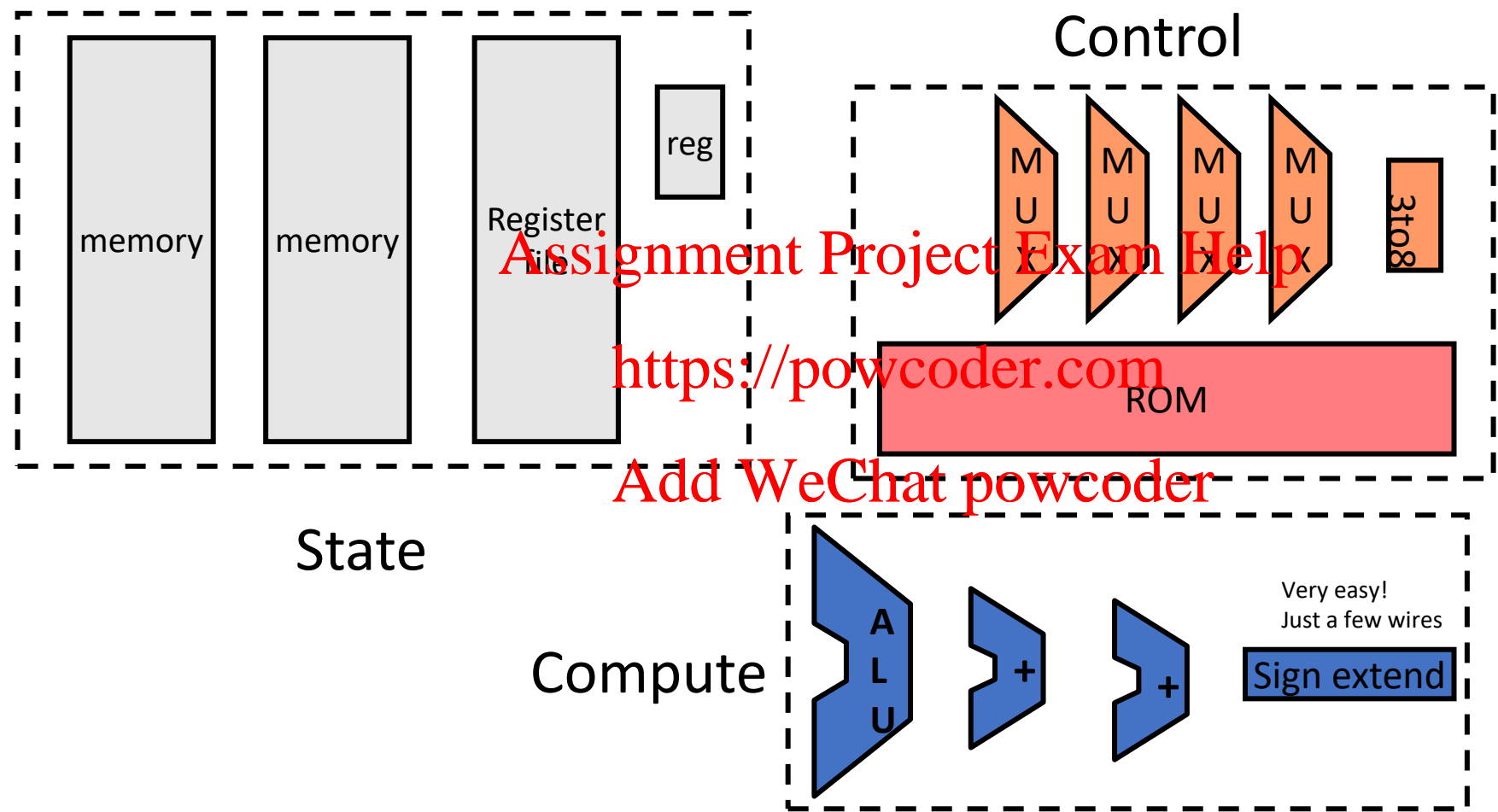

Here are the pieces, go build yourself a processor!

Control Building Blocks (1)

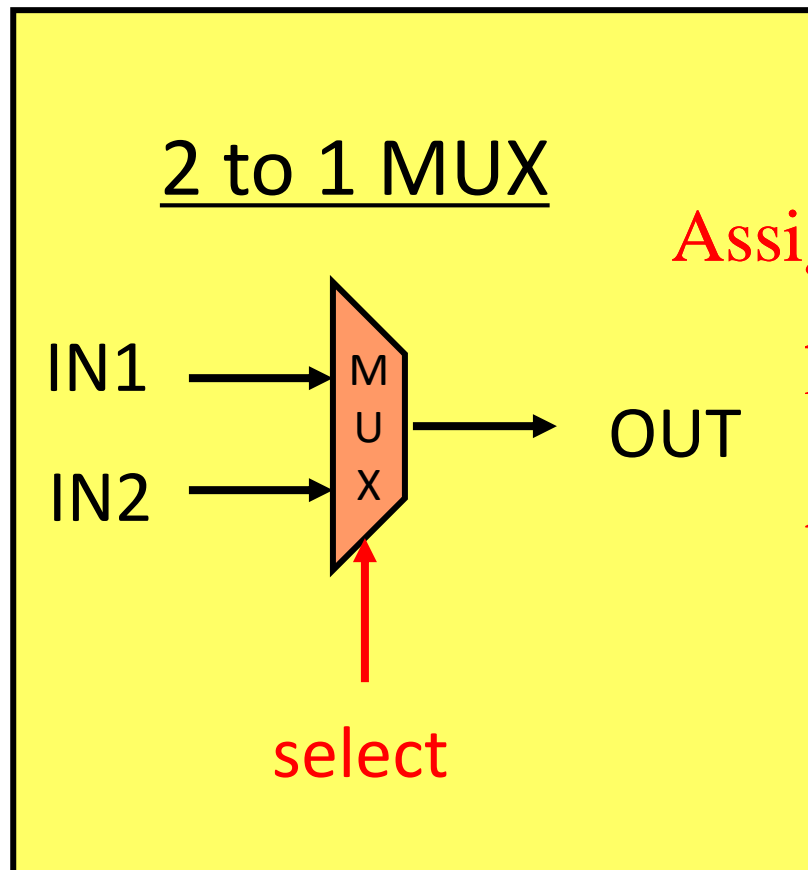

Connect one of the inputs
to OUT based on the value
of select

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


If (! select)

OUT = IN1

Else

OUT = IN2

Control Building Blocks (2)

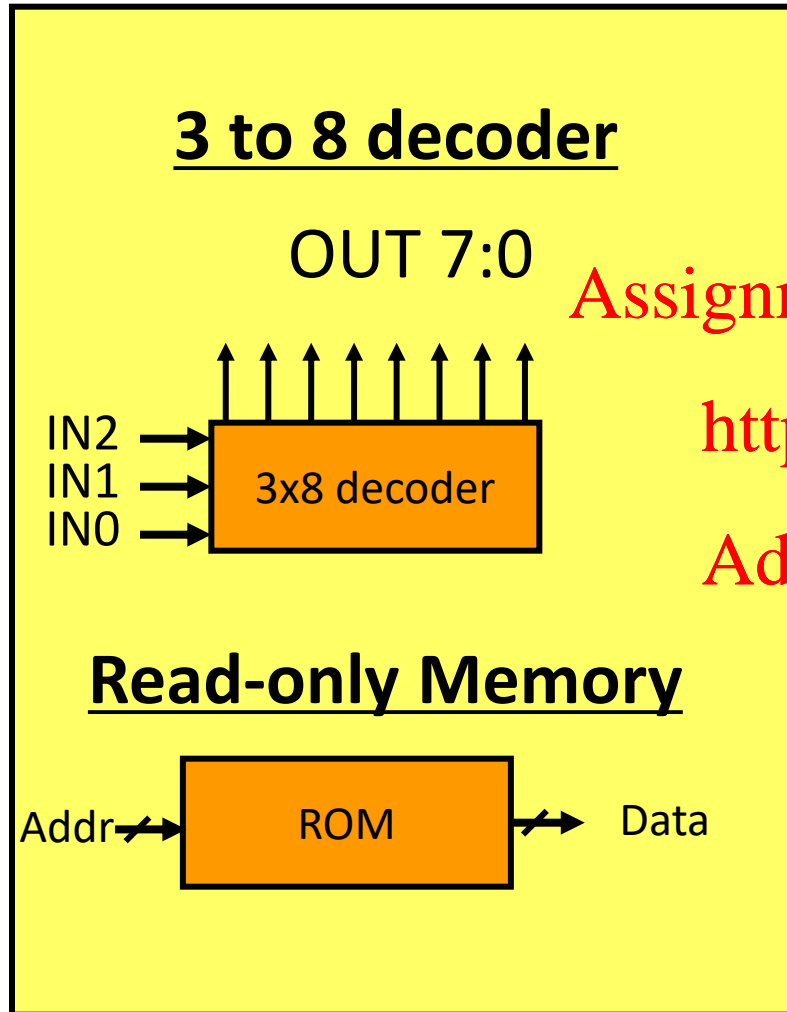


Decoder activates one of the output lines based on the input

IN	OUT
000	00000001
001	00000010
010	00000100
011	00001000
etc.	

ROM stores preset data in each location.
Give address to access data.

Compute Building Blocks (1)

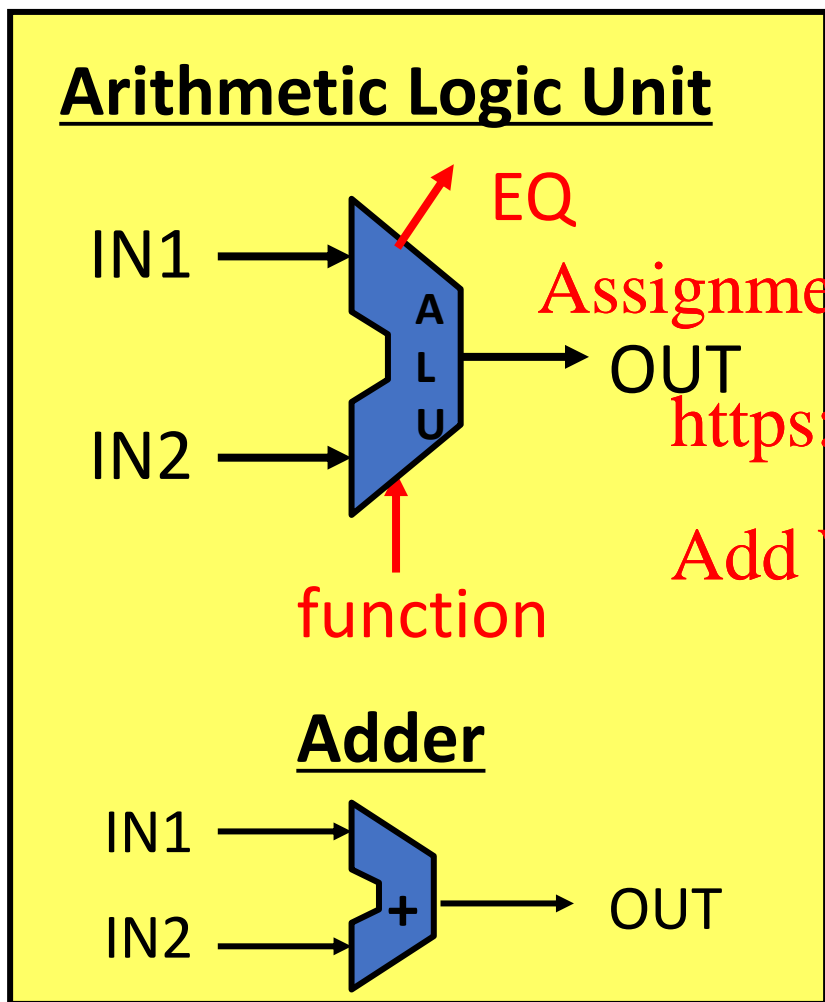

Perform basic arithmetic functions

$$OUT = f(IN1, IN2)$$

$$EQ = (IN1 == IN2)$$

For LC2K:


f=0 is add

f=1 is nor

For other processors, there are many more functions.

Just adds

Compute Building Blocks (2)

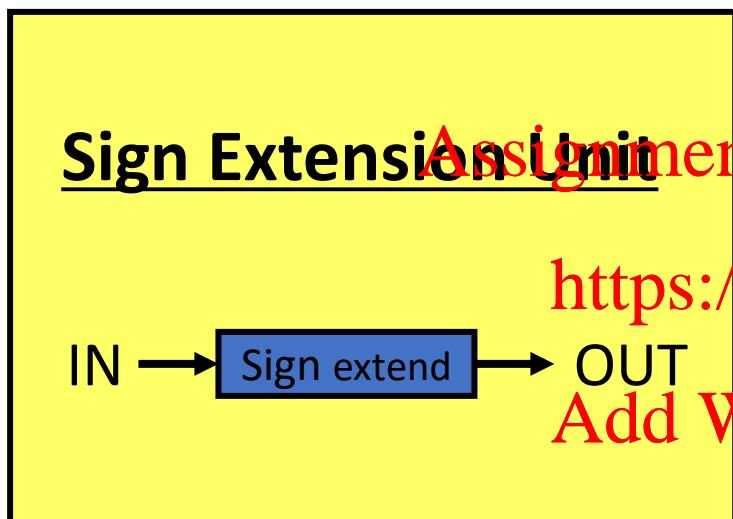

Sign extend input by
replicating the MSB to
width of output

<https://powcoder.com>

Add WeChat powcoder


$$\text{OUT}(31:0) = \text{SE}(\text{IN}(15:0))$$

$$\text{OUT}(31:16) = \text{IN}(15)$$

$$\text{OUT}(15:0) = \text{IN}(15:0)$$

Useful when compute unit is wider than data

State Building Blocks (1)

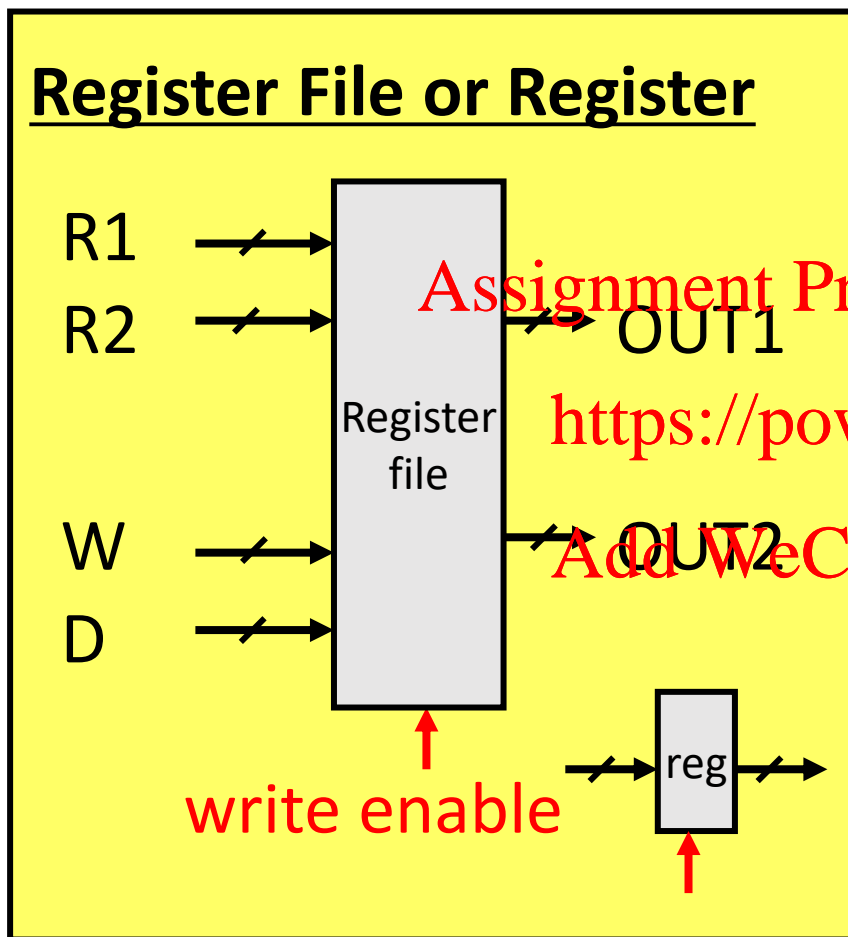

Small/fast memory to store temporary values

n entries (LC2 = 8)

r read ports (LC2 = 2)


w write ports (LC2 = 1)

* R_i specifies register number to read

* W specifies register number to write

* D specifies data to write

State Building Blocks (2)

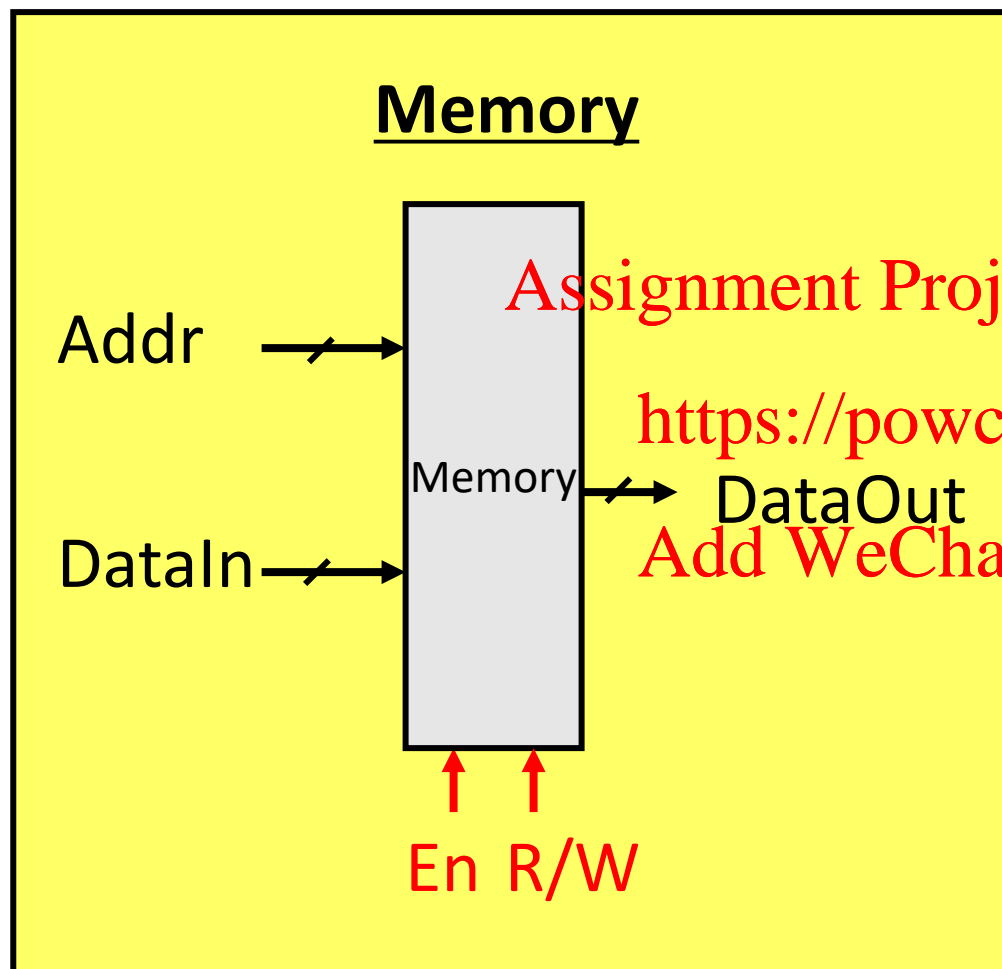


Slower storage structure to hold large amounts of stuff.

Use 2 memories for LC2

- * Instructions
- * Data
- * 65,536 total words


Review: LC2K Instruction Formats

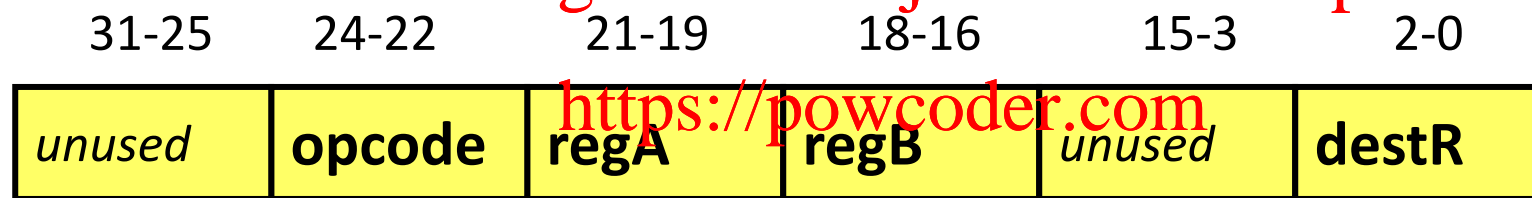- Tells you which bit positions mean what
- R-type instructions (opcodes add 000, nor 001)



Add WeChat powcoder

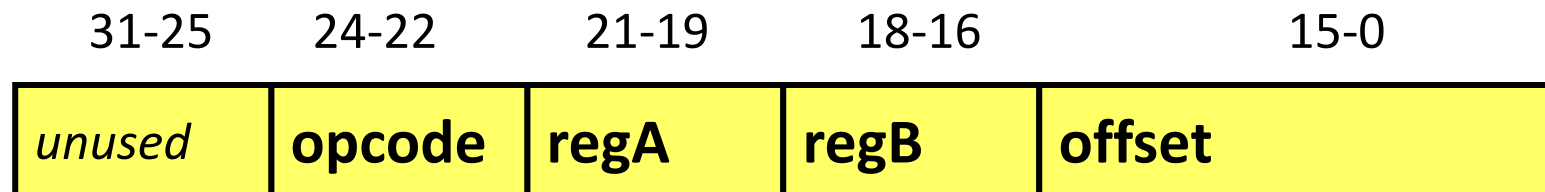- I-type instructions (opcodes lw 010, sw 011, beq 100)



Logistics

- There are 3 videos for lecture 10
 - L10_1 – Finite-State-Machines_Implementation
 - L10_2 – Single-Cycle-Processor
 - L10_3 – LC2K-Datapath
- There is one worksheet for lecture 10
 1. Finite state machine

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



L10_3 LC2K-Datapath

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder

Learning Objectives

- Ability to trace and explain the flow of data in a single-cycle processor diagram, using the blocks from the previous lecture.
- Identify the timing and operation of control circuit for a single-cycle processor.


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


LC2Kx Datapath Implementation

Single-Cycle

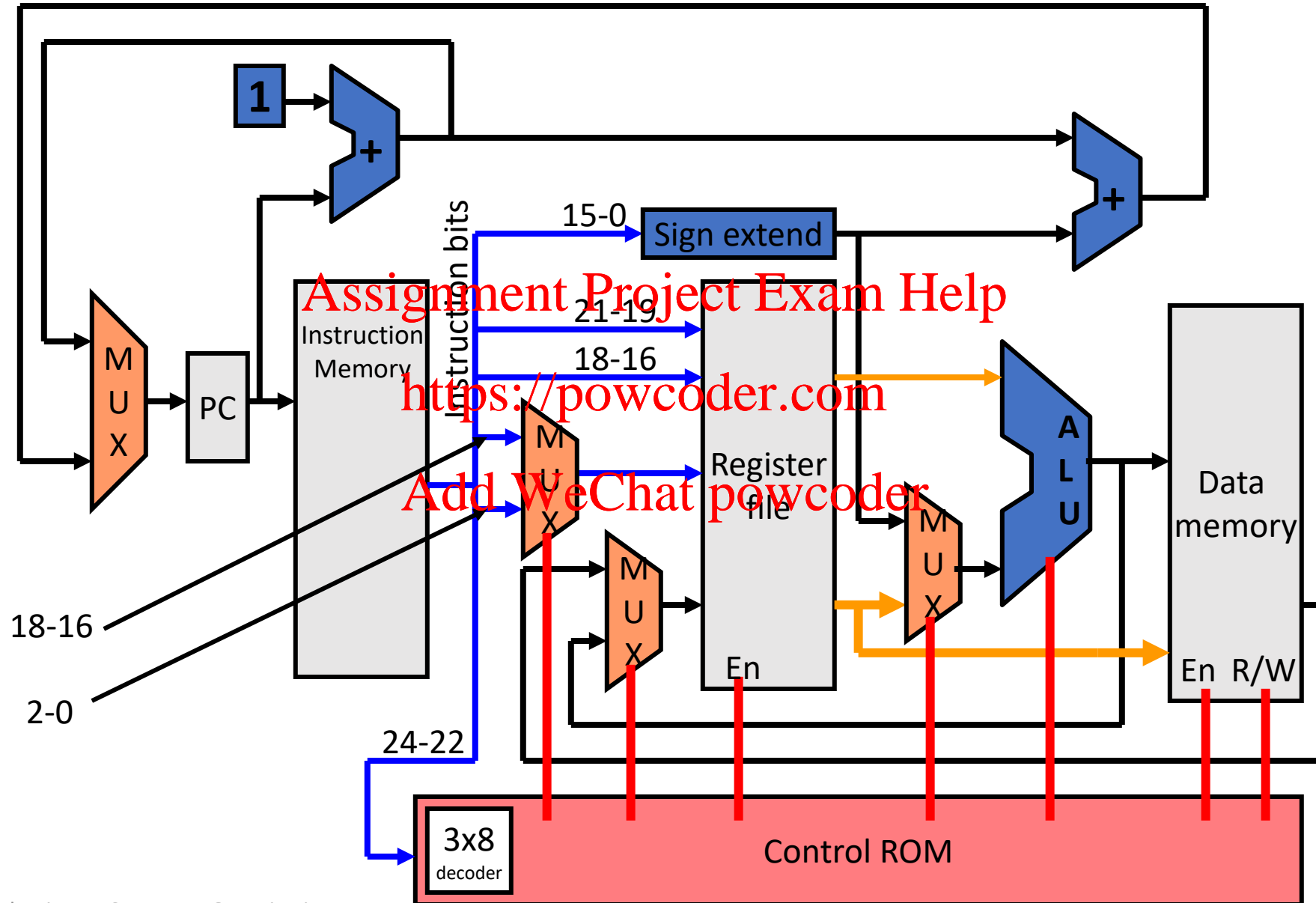


Executing an **ADD** Instruction

Single-Cycle

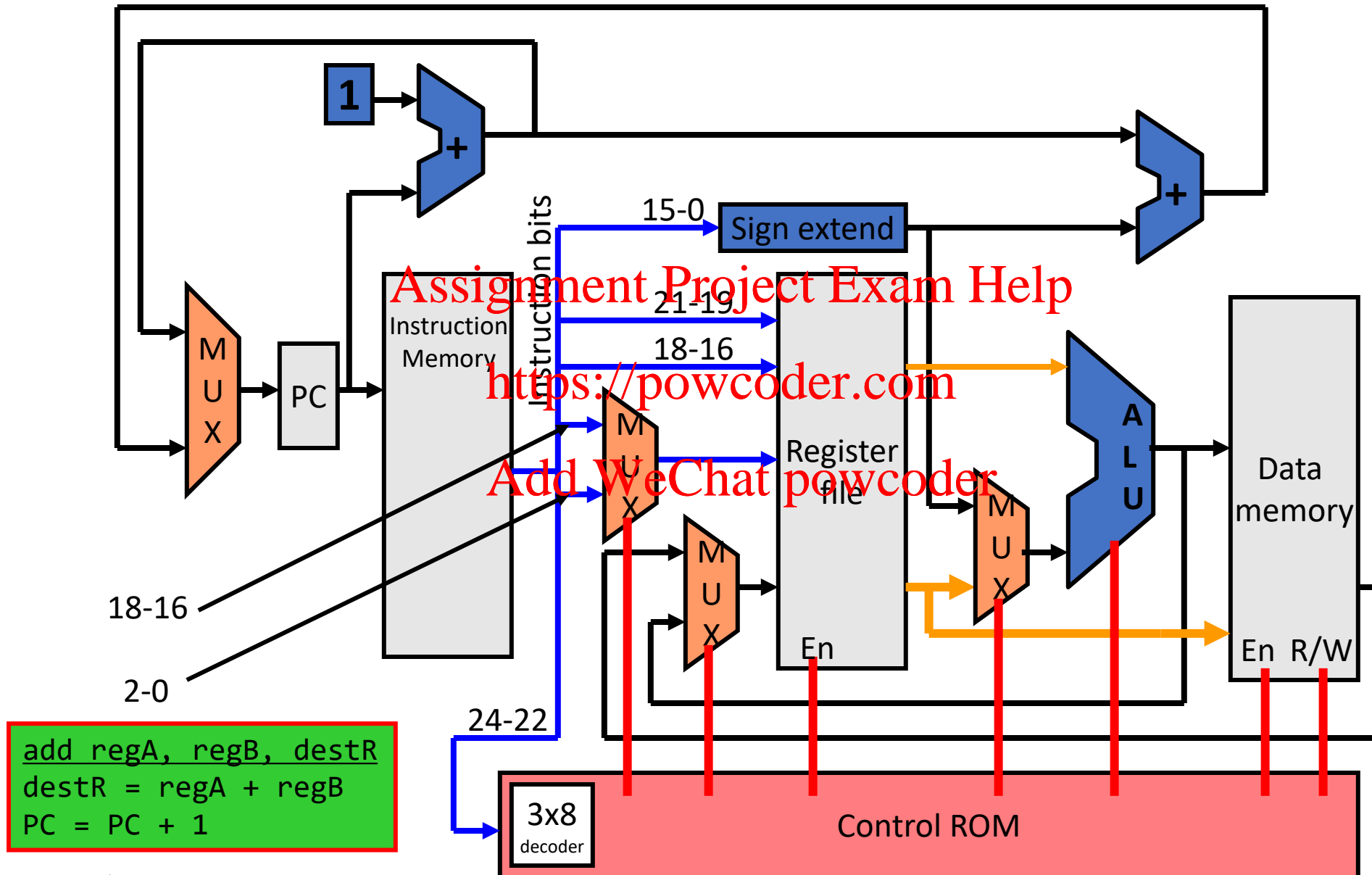

Executing a **NOR** Instruction


Single-Cycle

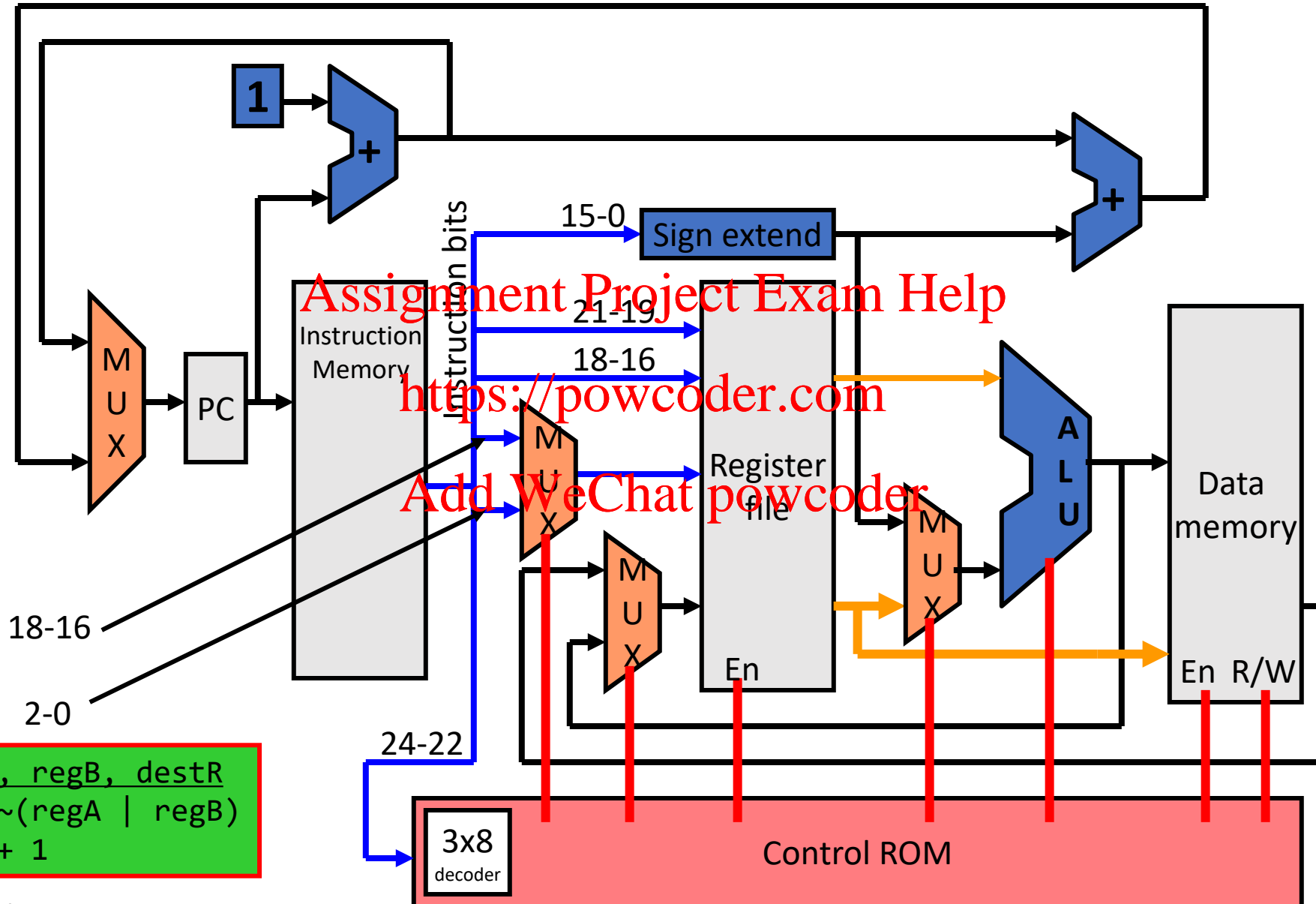

```
nor regA, regB, destR  
destR = ~(regA | regB)  
PC = PC + 1
```


Executing an **LW** Instruction

Single-Cycle

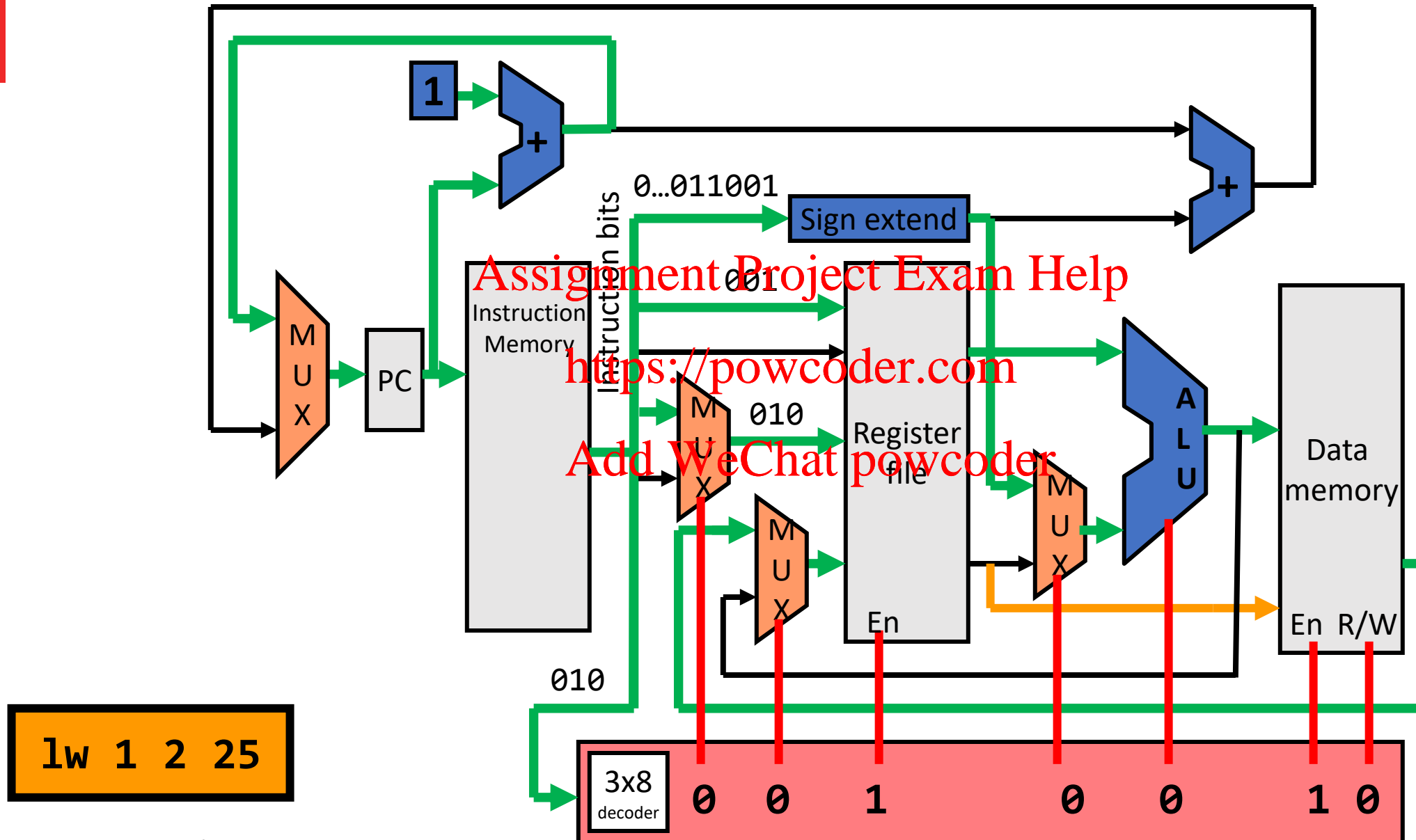



Assignment Project Exam Help

<https://powcoder.com>

More instructions to come...
Add WeChat powcoder

Next lecture!

Logistics

- There are 3 videos for lecture 10
 - L10_1 – Finite-State-Machines_Implementation
 - L10_2 – Single-Cycle-Processor
 - L10_3 – LC2K-Datapath
- There is one worksheet for lecture 10
 1. Finite state machine

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder