



L9_1 Combinational-Logic- Timing

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder



Learning Objectives

- To identify the propagation delay in combinational logic circuits.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Combinational Circuits Implement Boolean Expressions


- Output is determined exclusively by the input
- No memory: Output is valid only as long as input is
 - Adder is the basic gate of the ALU (this lecture)
 - Decoder is the basic gate of indexing (we will use this next lecture)
 - MUX is the basic gate controlling data movement

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder


Half-Adder

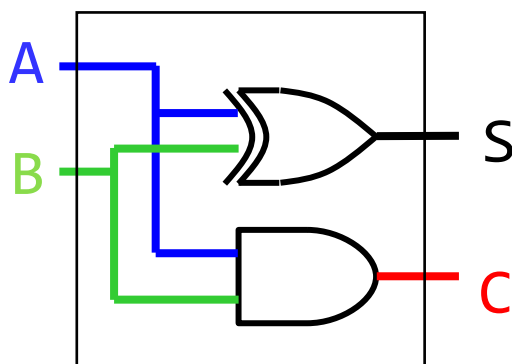

Decoder

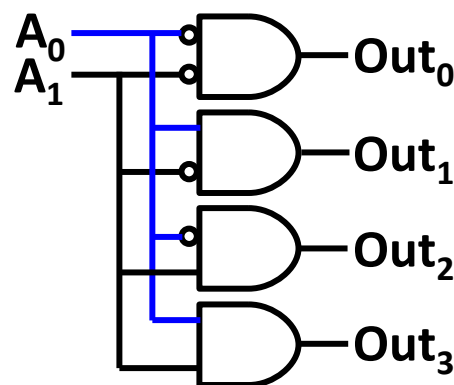


Mux

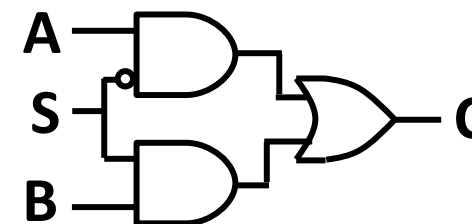

Propagation Delay in Combinational Gates

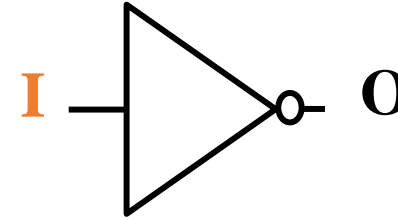- Gate outputs do not change exactly when inputs do.



- Transmission time over wires (~speed of light)
- Saturation time to make transistor gate switch


Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

Every combinatorial circuit has a propagation delay (time between input and output stabilization)

ideal
real

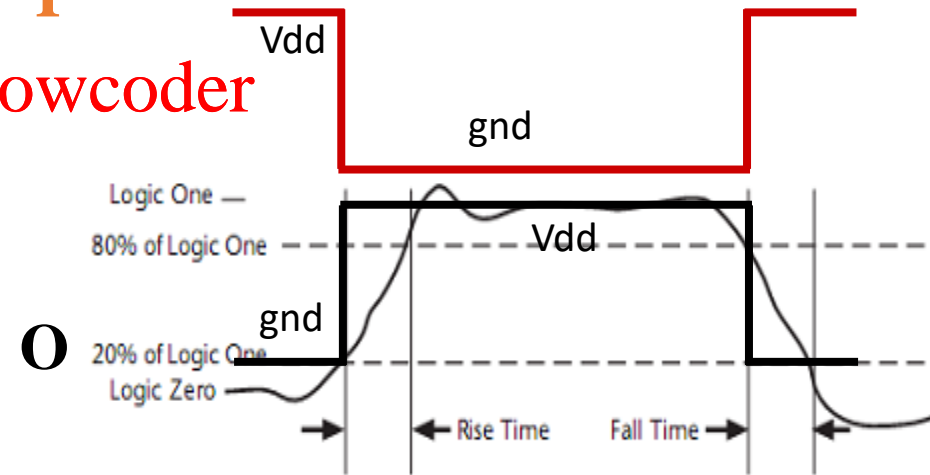


Timing in Combinational Circuits

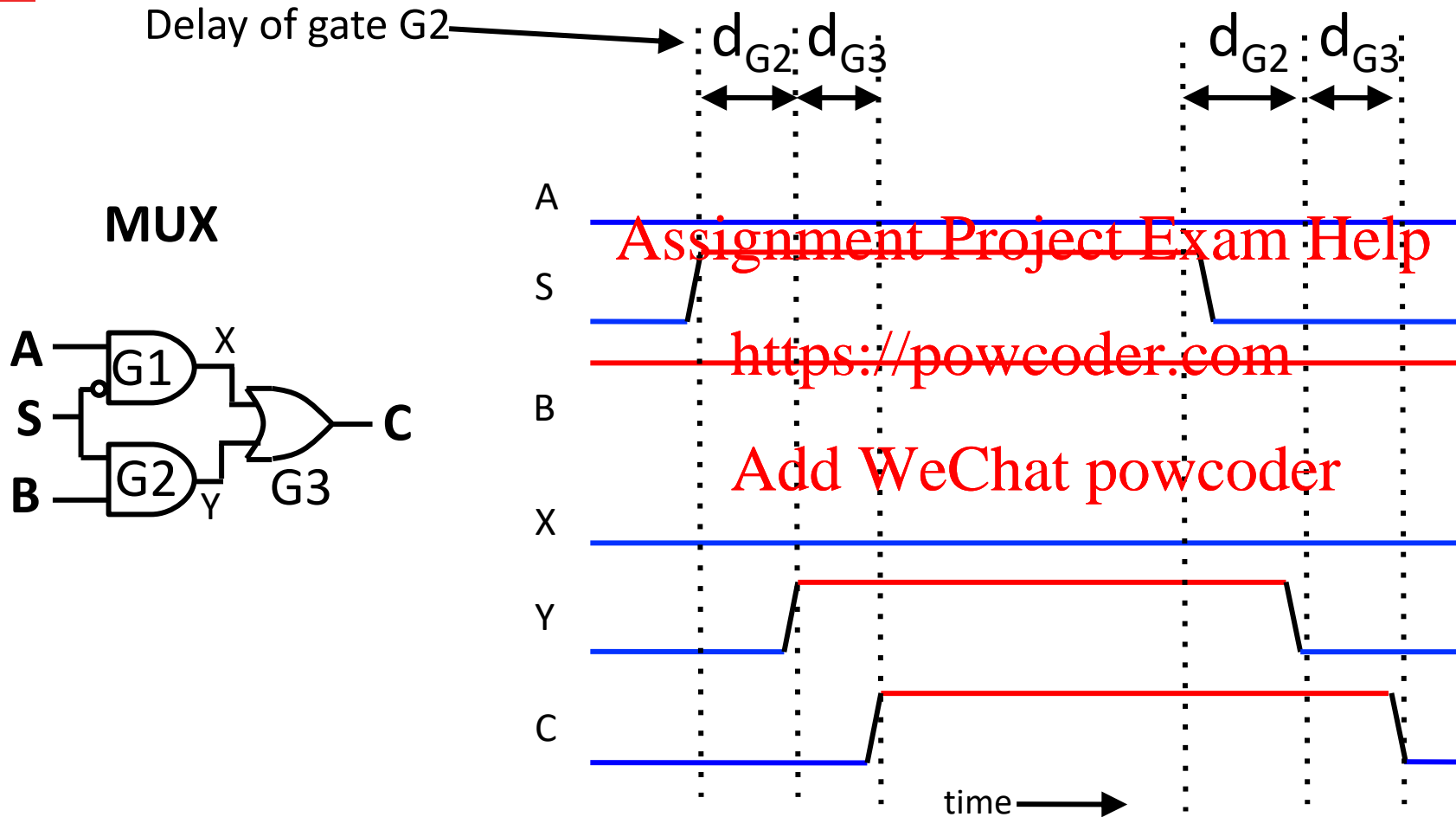

What is the input/output delay (or simply, delay) of the MUX?


Waveform viewers are part of designers' daily life

Comb.
Logic

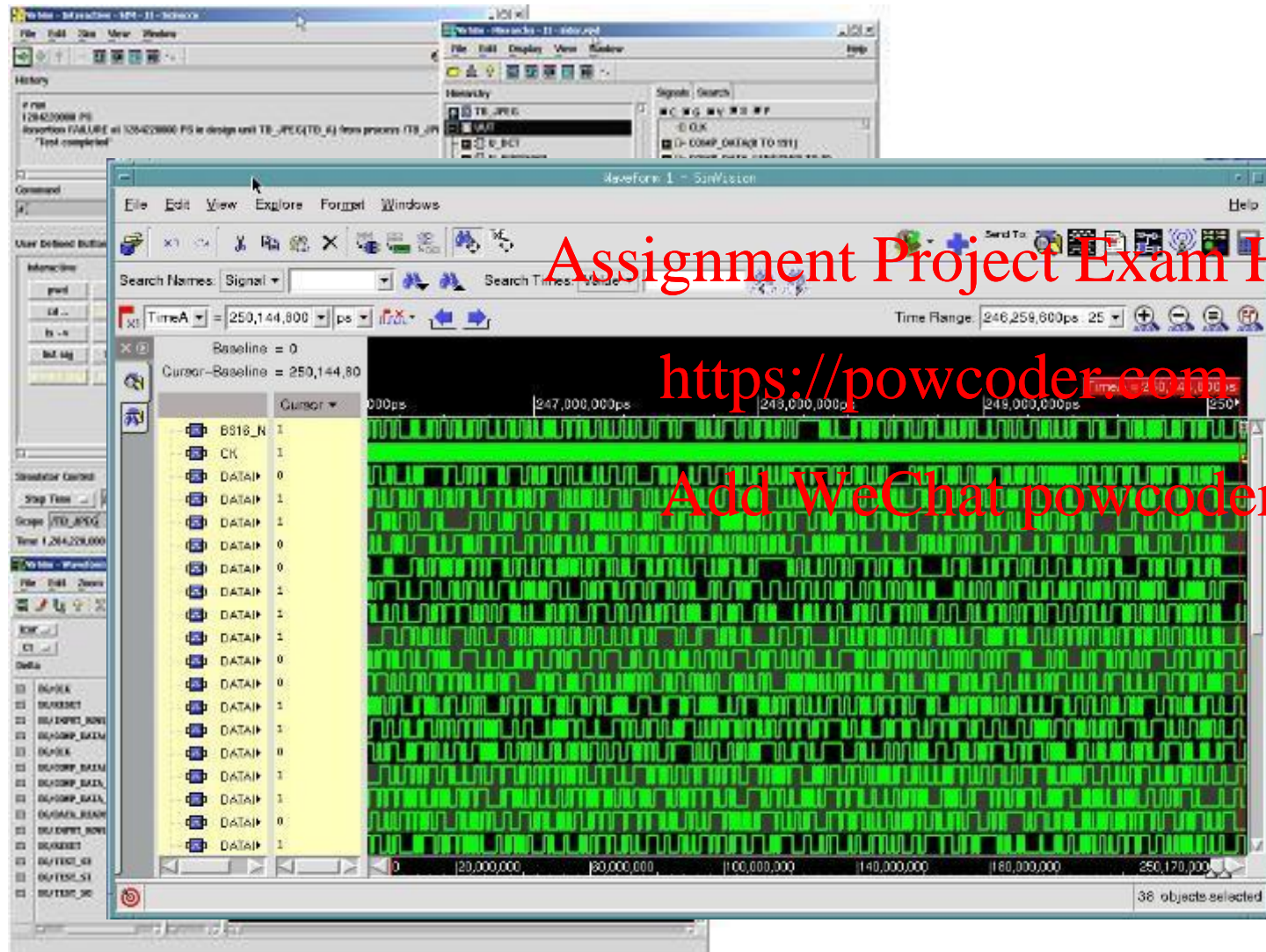

What is the delay of this Circuit?

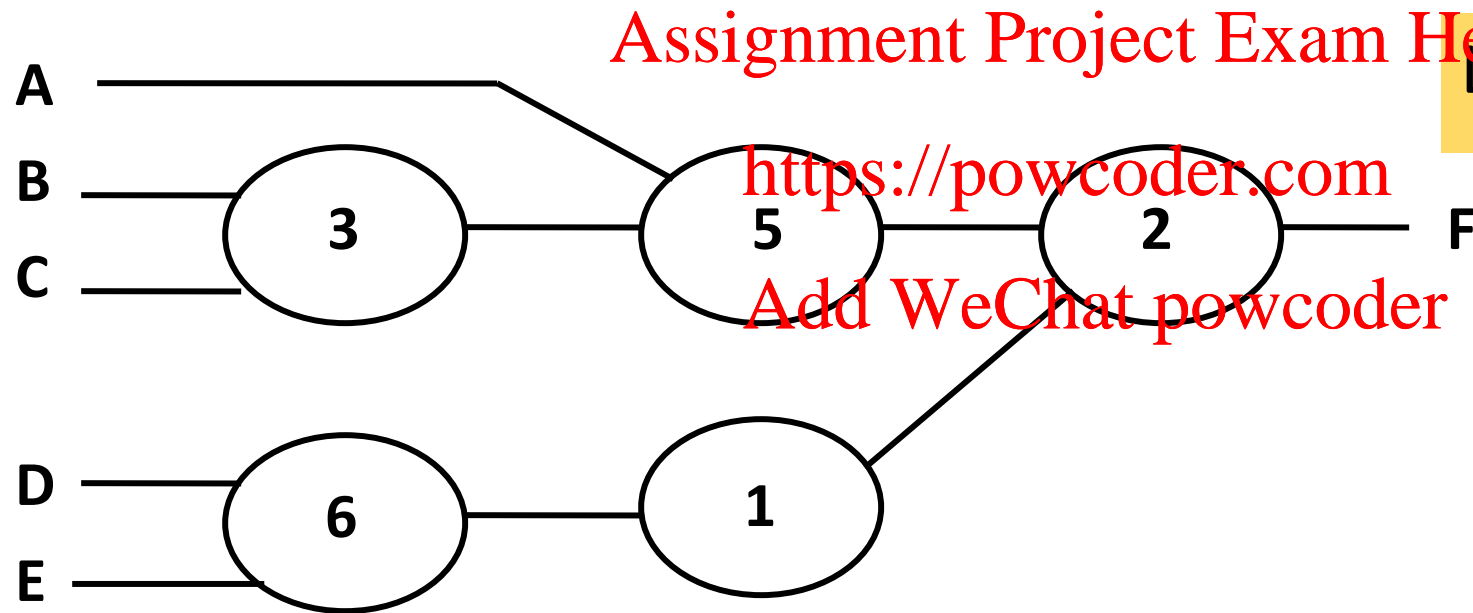Each oval represents one gate (the type does not matter)
= delay of each gate



Longest path: $3 + 5 + 2 = 10$

Example: Building a Circuit

Problem: Build an ALU (Arithmetic Logic Unit) for LC-2K

- Use some of the blocks we have learned about so far to build a circuit




- Using - full adder, NOR, mux
- Input A, 32 bits
- Input B, 32 bits
- Input S, 1 bit
- Output, 32 bits
- When S is low, the output is A+B, when S is high, the output is NOR(a, b)

Assignment Project Exam Help



<https://powcoder.com>

Add WeChat powcoder

32 wires

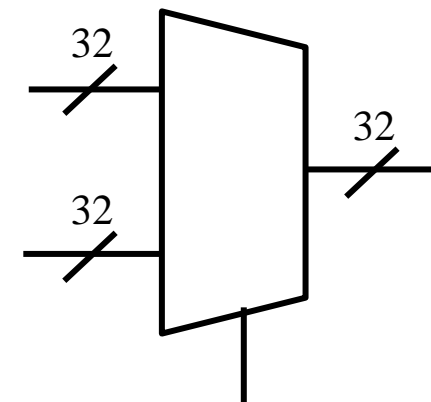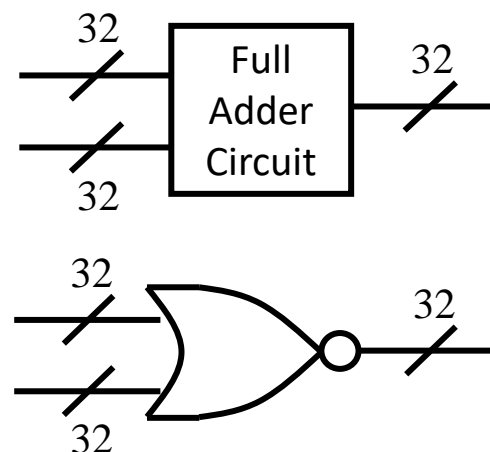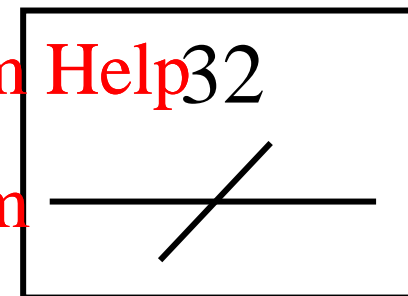

LC-2K ALU (Arithmetic Logic Unit)

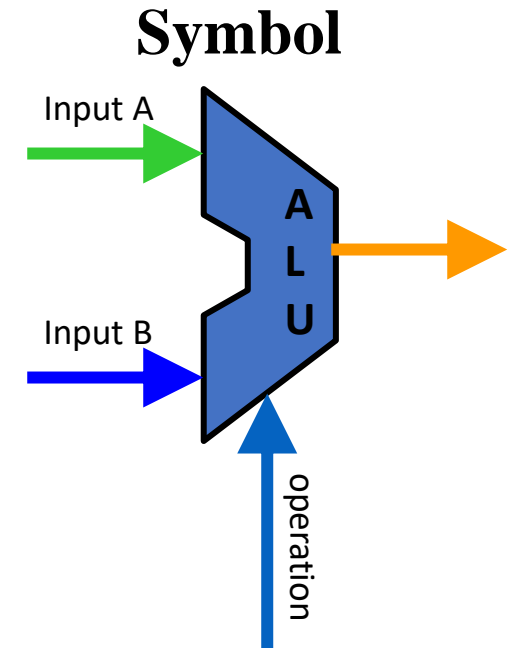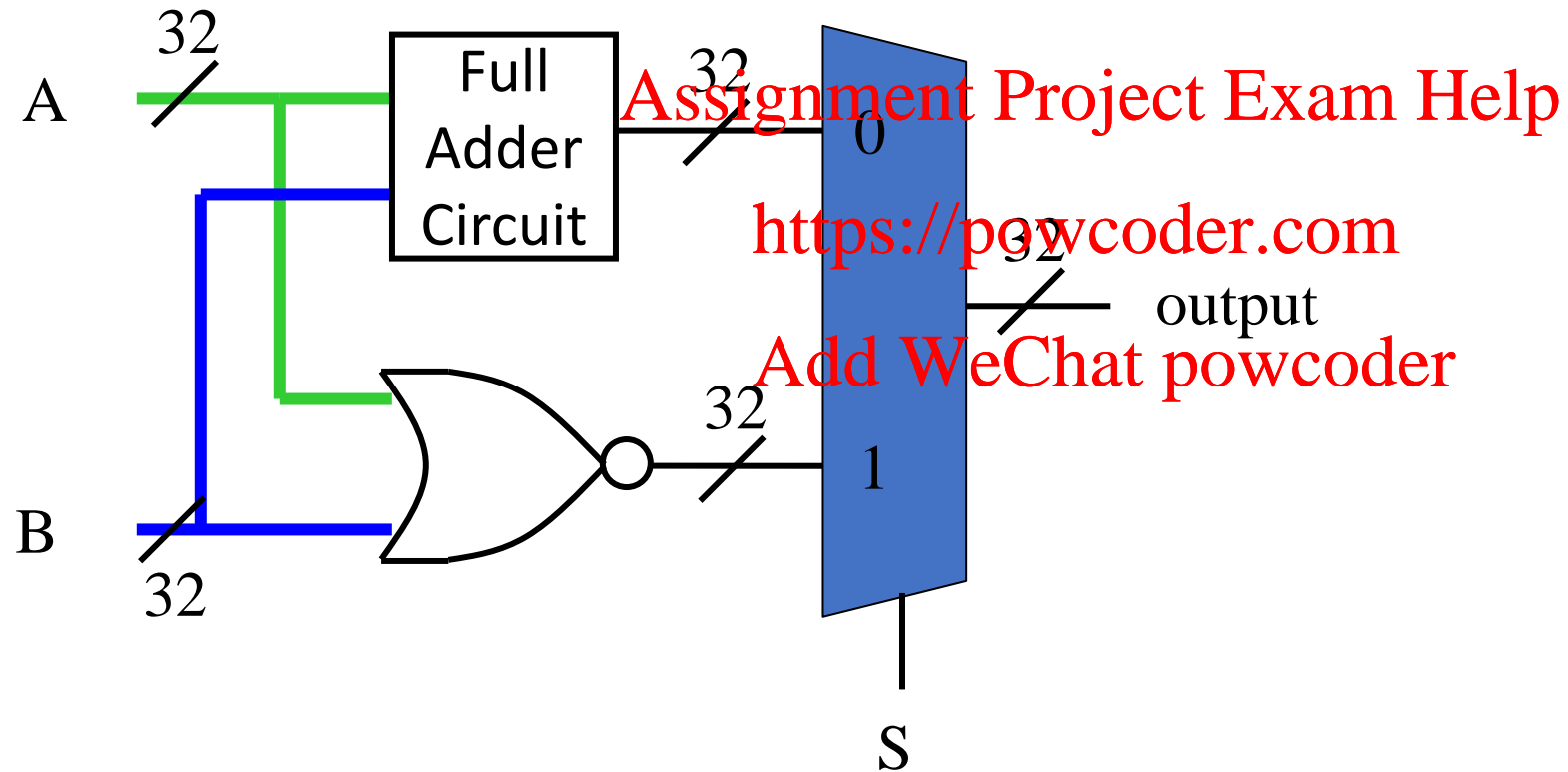


Logistics

- There are 3 videos for lecture 9
 - L9_1 – Combinational-Logic-Timing
 - L9_2 – Memory_Latches-Clocks
 - L9_3 – Finite-State-Machines
- There are two worksheet for lecture 9
 1. Circuit design – combinational logic – you are ready for this now
 2. Circuit design – sequential logic

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



L9_2 Memory_Latches-Clocks

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder

Learning Objectives

- To identify and understand the operation of simple devices to retain memory in circuits.
- To understand the inclusion of timing with the clock circuit

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Assignment Project Exam Help

Sequential logic:

<https://powcoder.com>

Add WeChat powcoder

giving memory to circuits

What is sequential logic?

- So far, we've covered combinational
 - Output is determined from input
 - But computers don't work that way — they have state
- Examples of state
 - Registers
 - Memory
- Sequential logic's output depends not only on the current input, but also on its current state
- This lecture will show you how to build sequential logic from gates
 - The key is feedback


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Using Feedback to "Remember"

Sequential
Logic

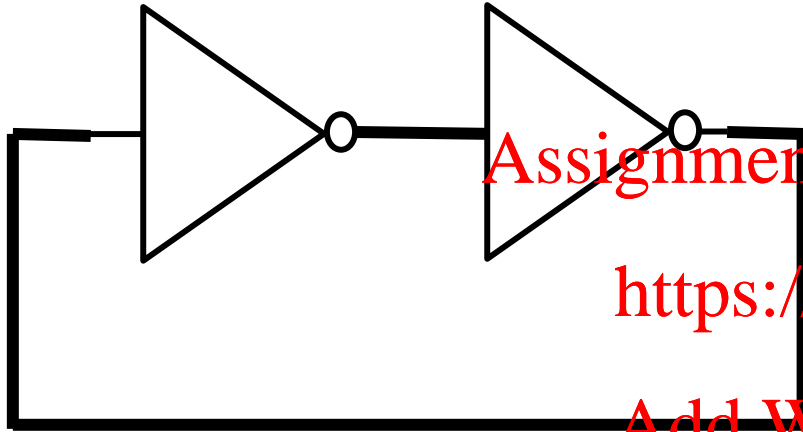

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

This remembers its initial value!

Very basic memory

What's wrong with this, though?

Your First Memory: S-R Latch

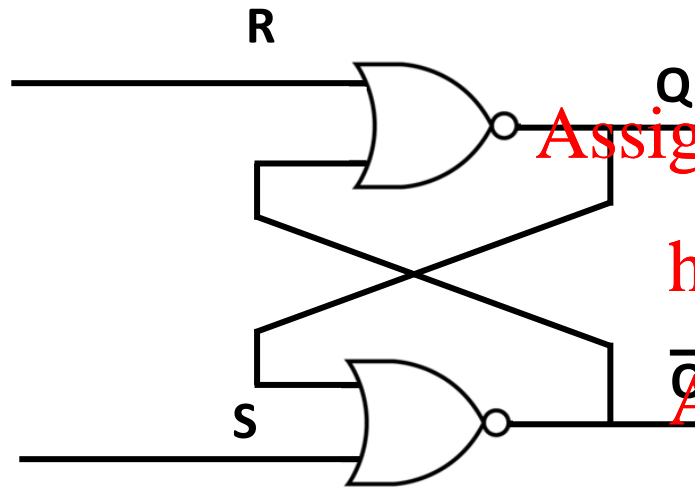

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

“high” is:

- logical 1
- 1 state
- “set”
- high voltage

“low” is:

- logical 0
- 0 state
- “Unset”
- low voltage


\bar{Q} is not Q

Sequential
Logic

- Output Q and \bar{Q} should have memory, i.e., retain their value for *some input changes*
- Output Q and \bar{Q} should always have opposite values

Your First Memory: S-R Latch

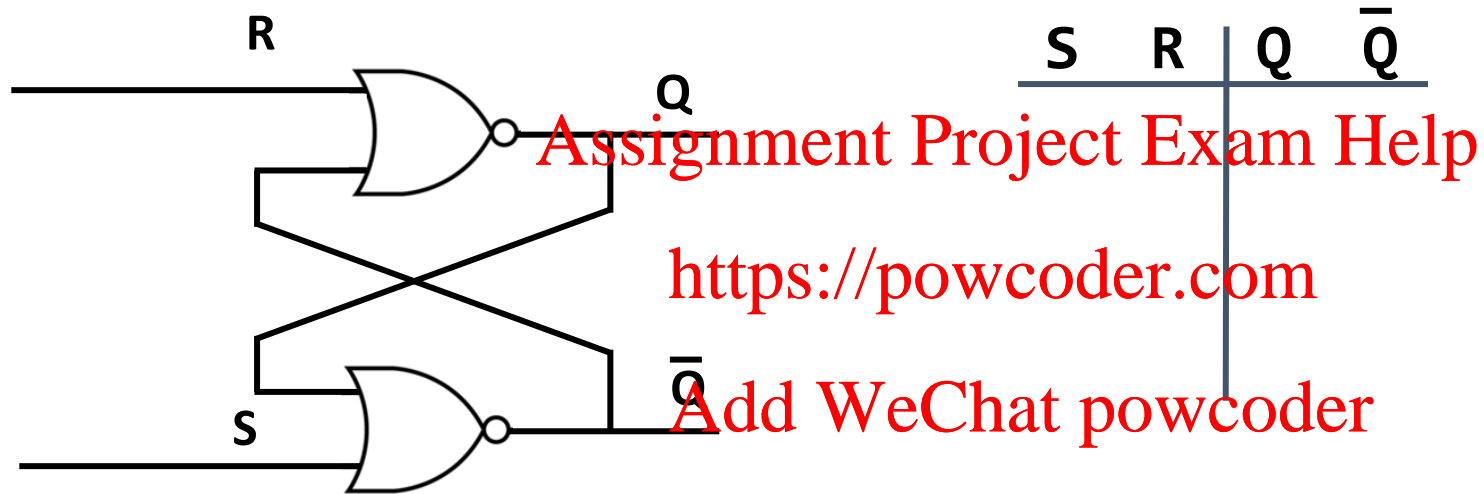
Problem: Create a truth table for this circuit



- Output Q and \bar{Q} should have memory, i.e., retain their value for *some input changes*
- Output Q and \bar{Q} should always have opposite values

Your First Memory: S-R Latch

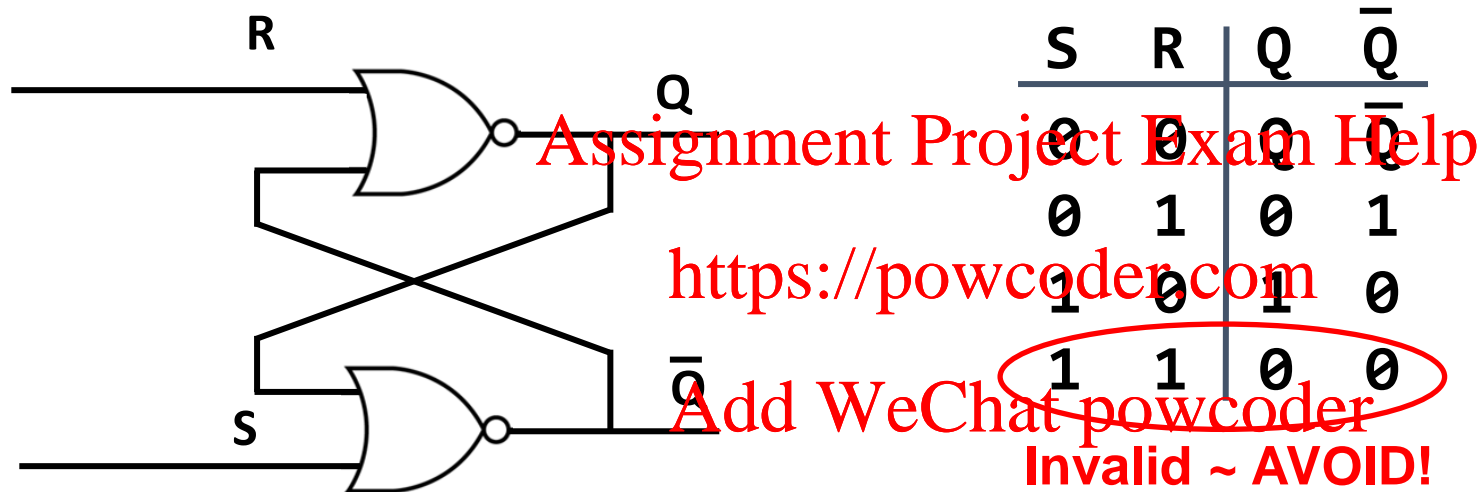
Problem: Create a truth table for this circuit



- Output Q and \bar{Q} should have memory, i.e., retain their value for *some input changes*
- Output Q and \bar{Q} should always have opposite values

Q and \bar{Q} are supposed to be opposite of each other, so **this is a state we avoid**. This state can also lead to unstable future states. Try setting $S = 0$ and $R = 0$ now!

D Latch

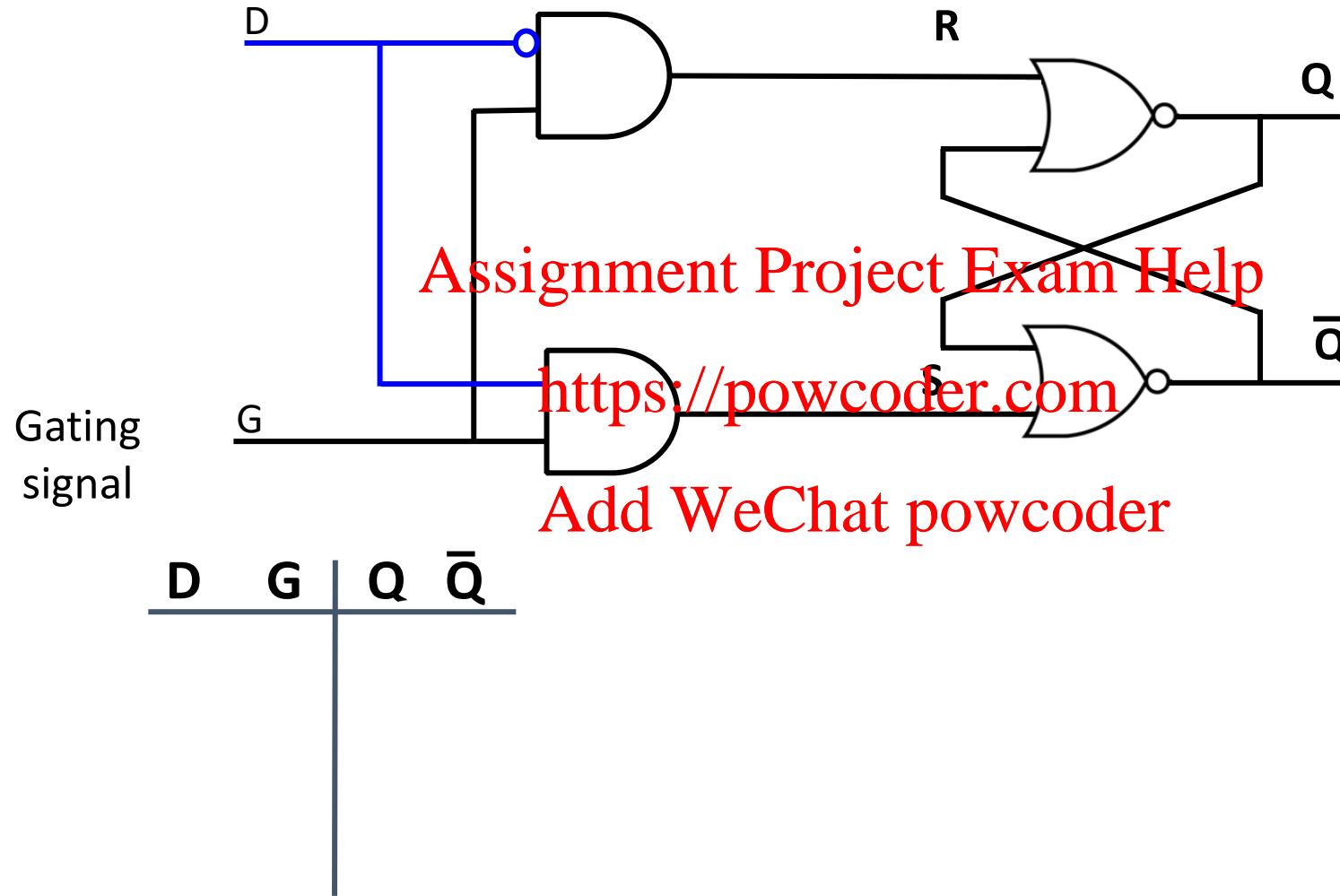


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


D Latch

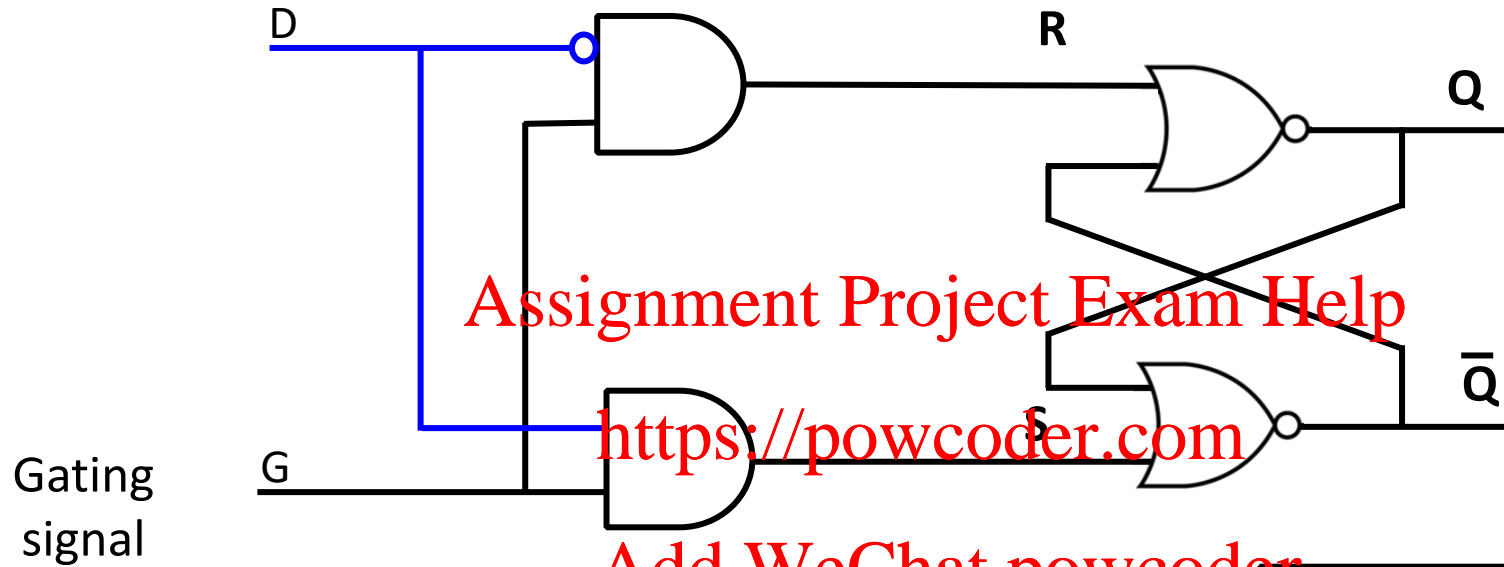



Next state is set

D	G	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	Q	\bar{Q}
1	1	1	0



Set state is retained when gate is low

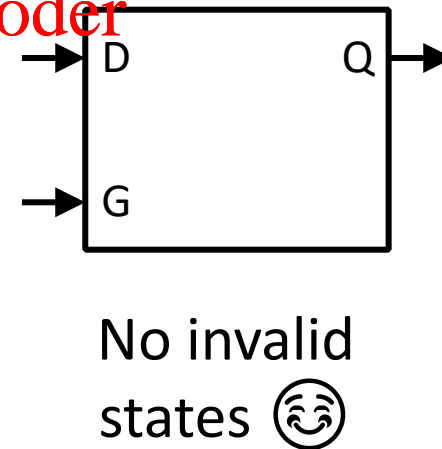

D Latch – Gate and Data

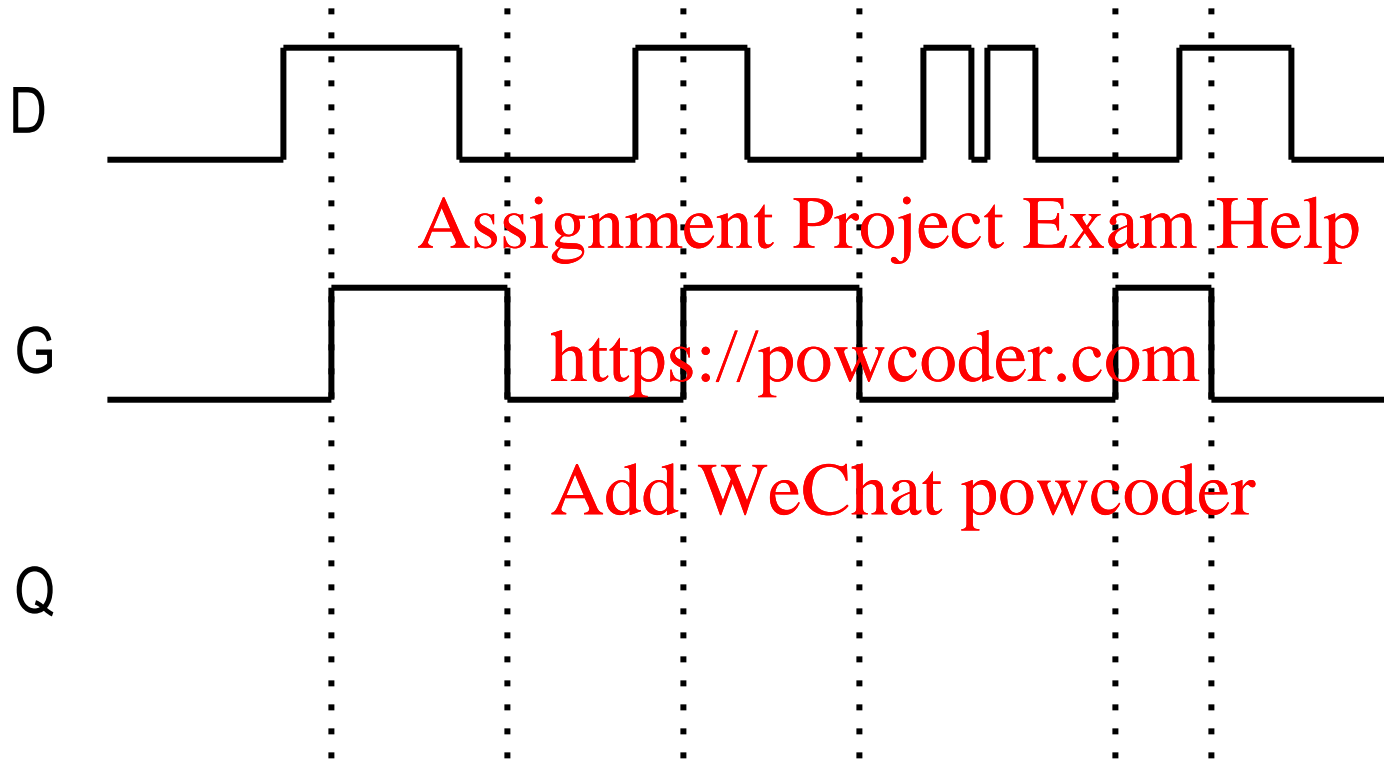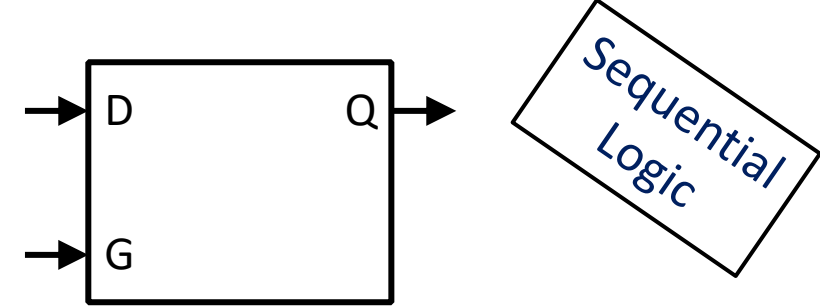

D Latch – Gate and Data

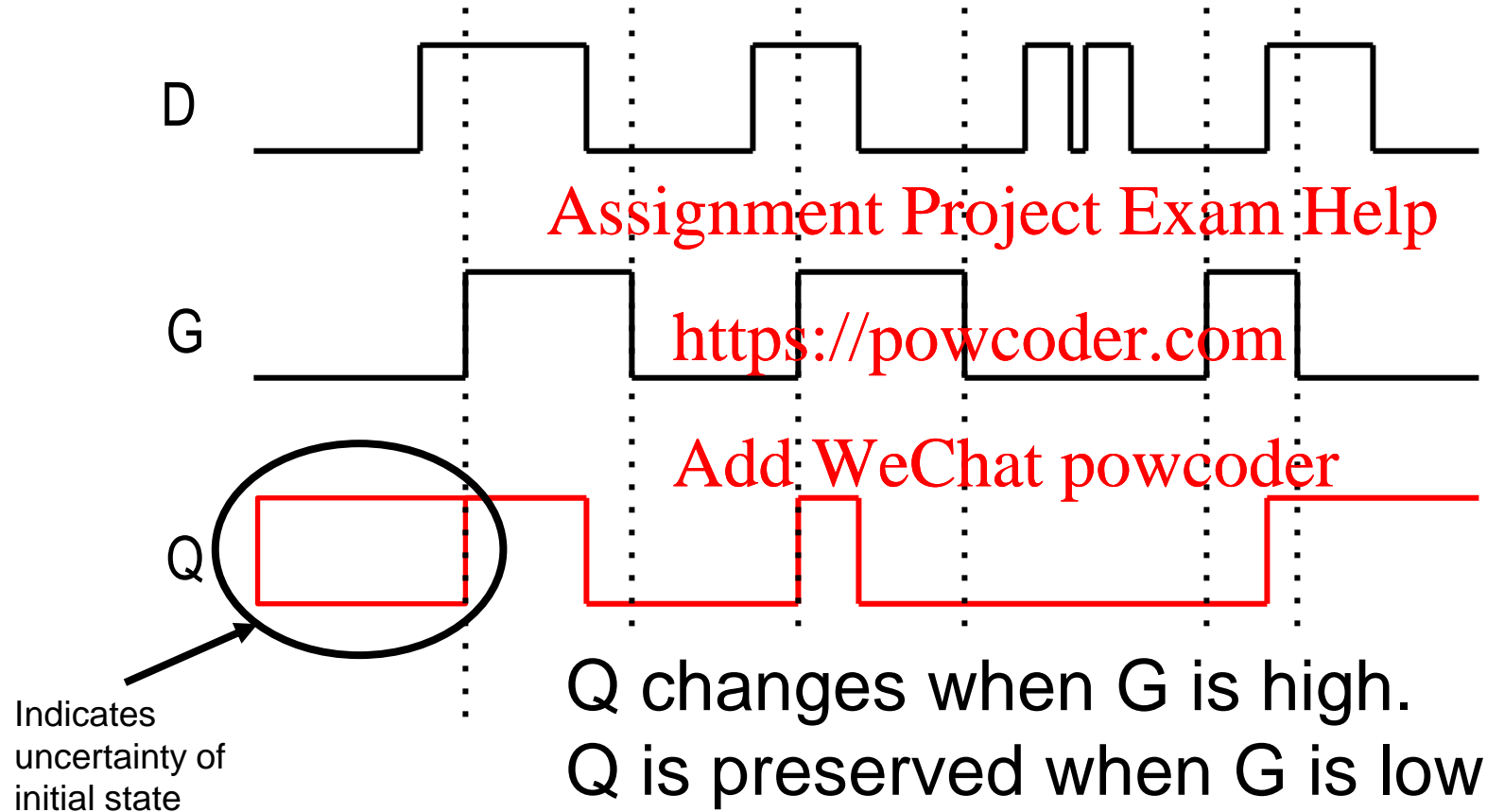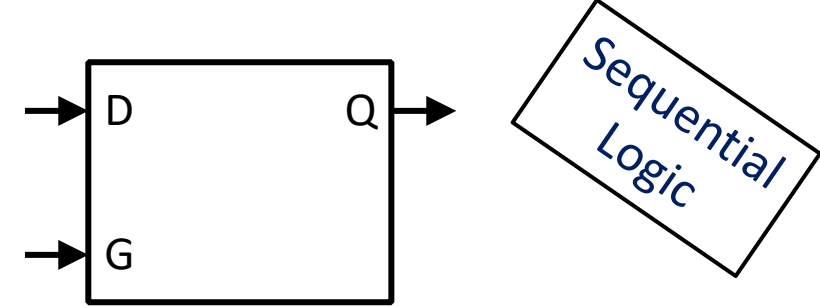


Adding a Clock to the Mix

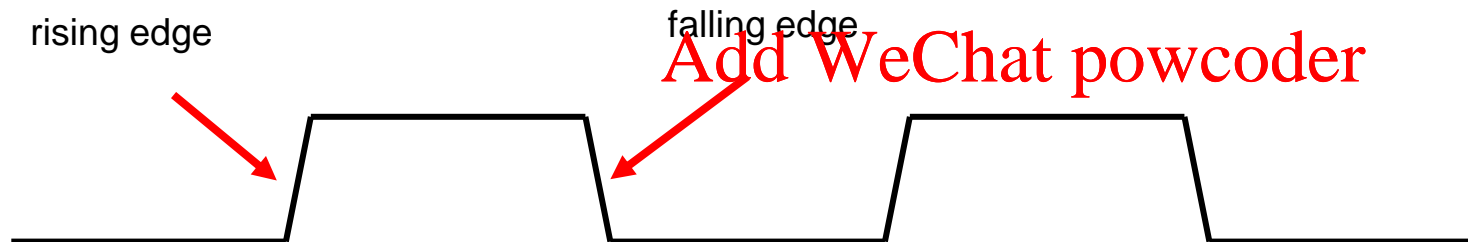
- Problem if we build complex circuits with feedback, these "latches" can become unstable when transparent
 - "Glitches" propagate around and around
 - Take 270 to learn more
- We can solve this if we introduce a clock
 - Alternating signal that switches between 0 and 1 states at a fixed frequency (e.g., 100MHz)
 - Only store the value the instant the clock changes
- What should the clock frequency be?
 - It depends on the longest propagation delay between state and next state combination logic
 - And a few other things outside of the scope of 370 (shout out 270)

Clocks

- Clock signal
 - Periodic pulse
 - Generated using oscillating crystal or ring oscillator
 - Distributed throughout chip using clock distribution net





Rising-Edge Triggered D Flip-Flop

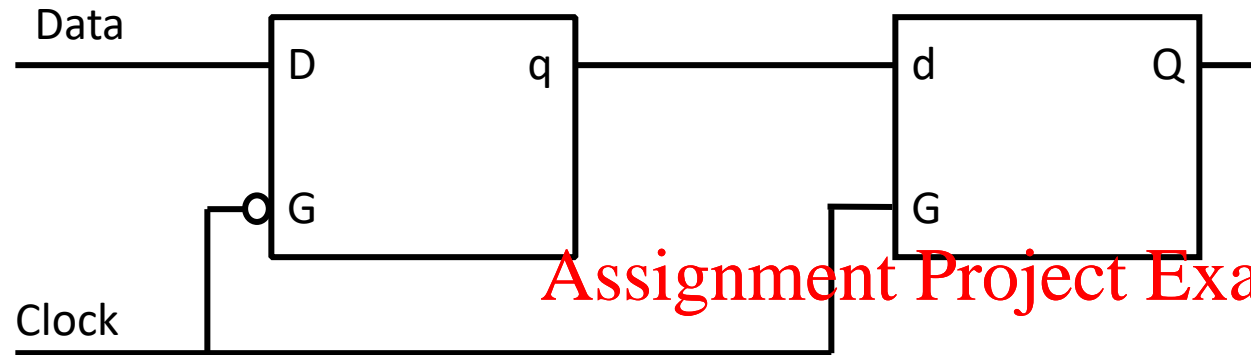

Assignment Project Exam Help



<https://powcoder.com>

Add WeChat powcoder

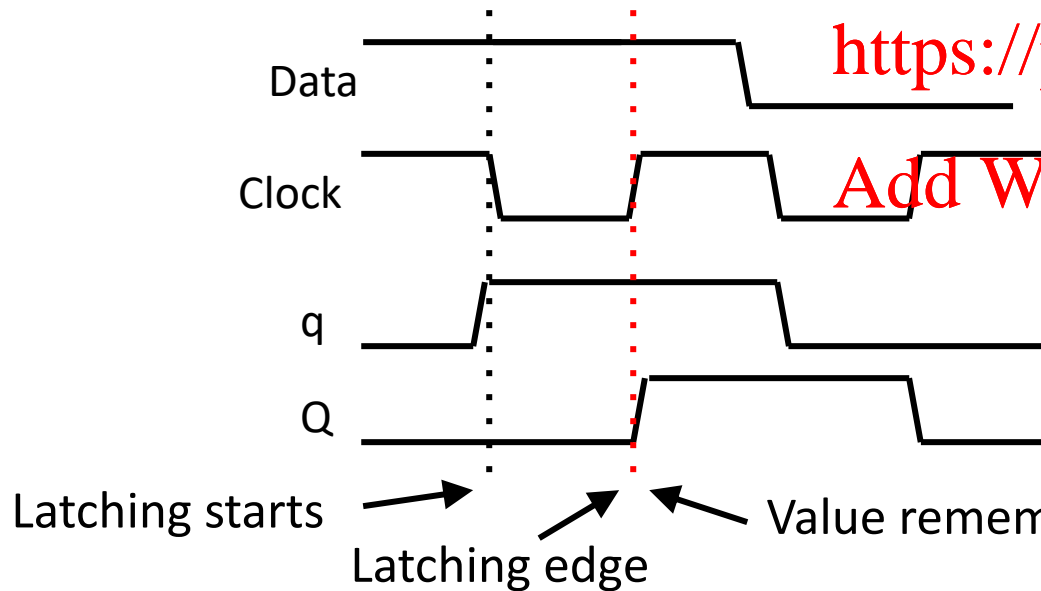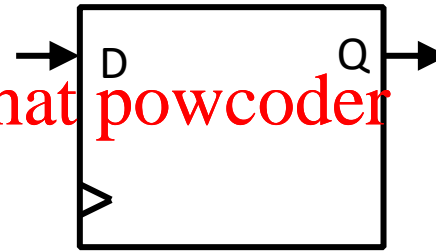



D Flip-Flop – Clock and Data

Sequential
Logic

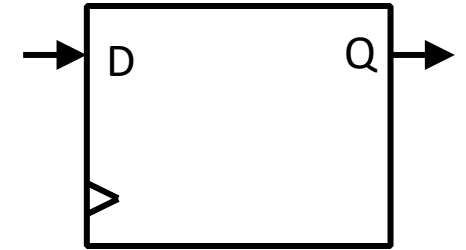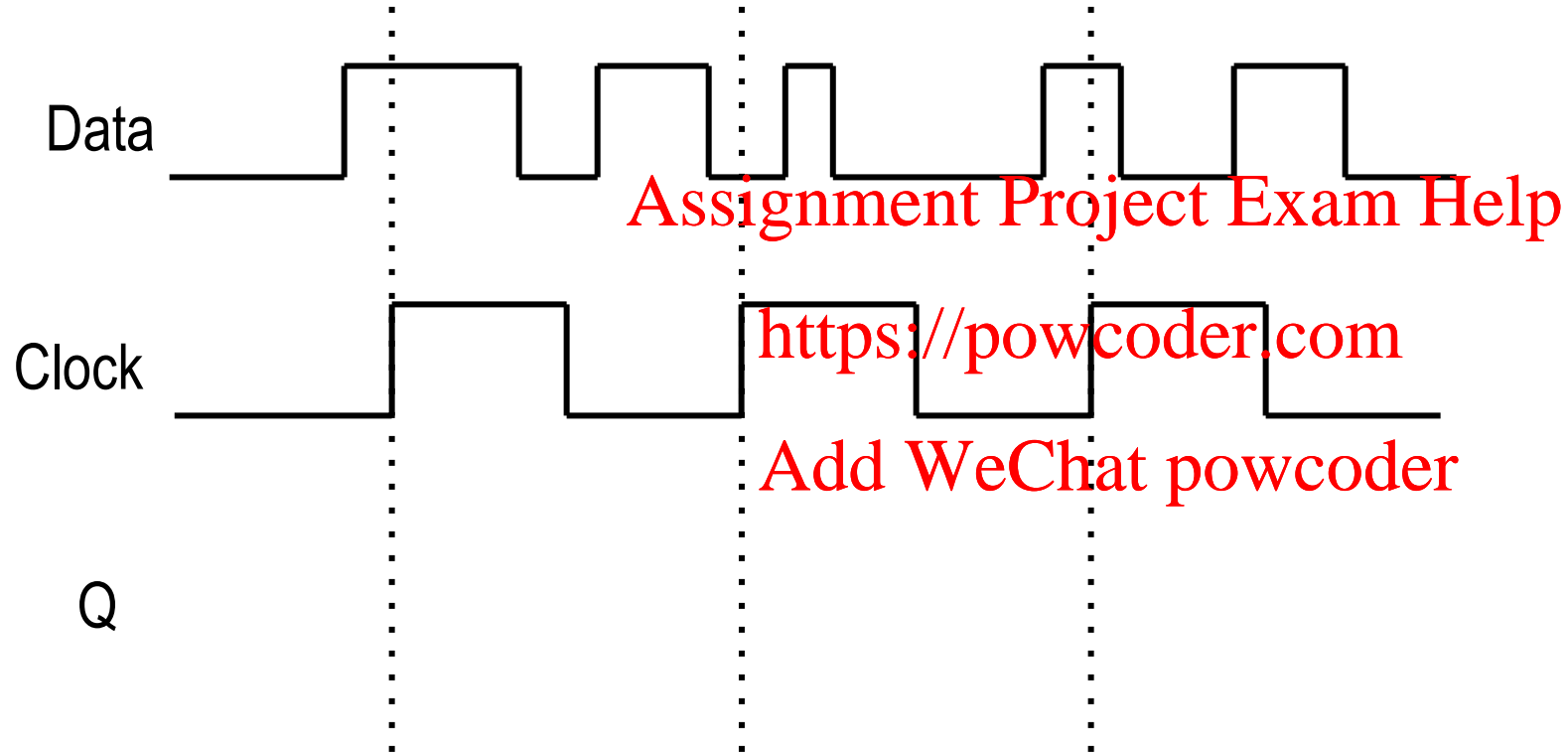



D Flip-Flop – Clock and Data

Sequential
Logic

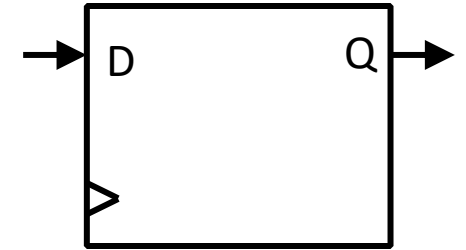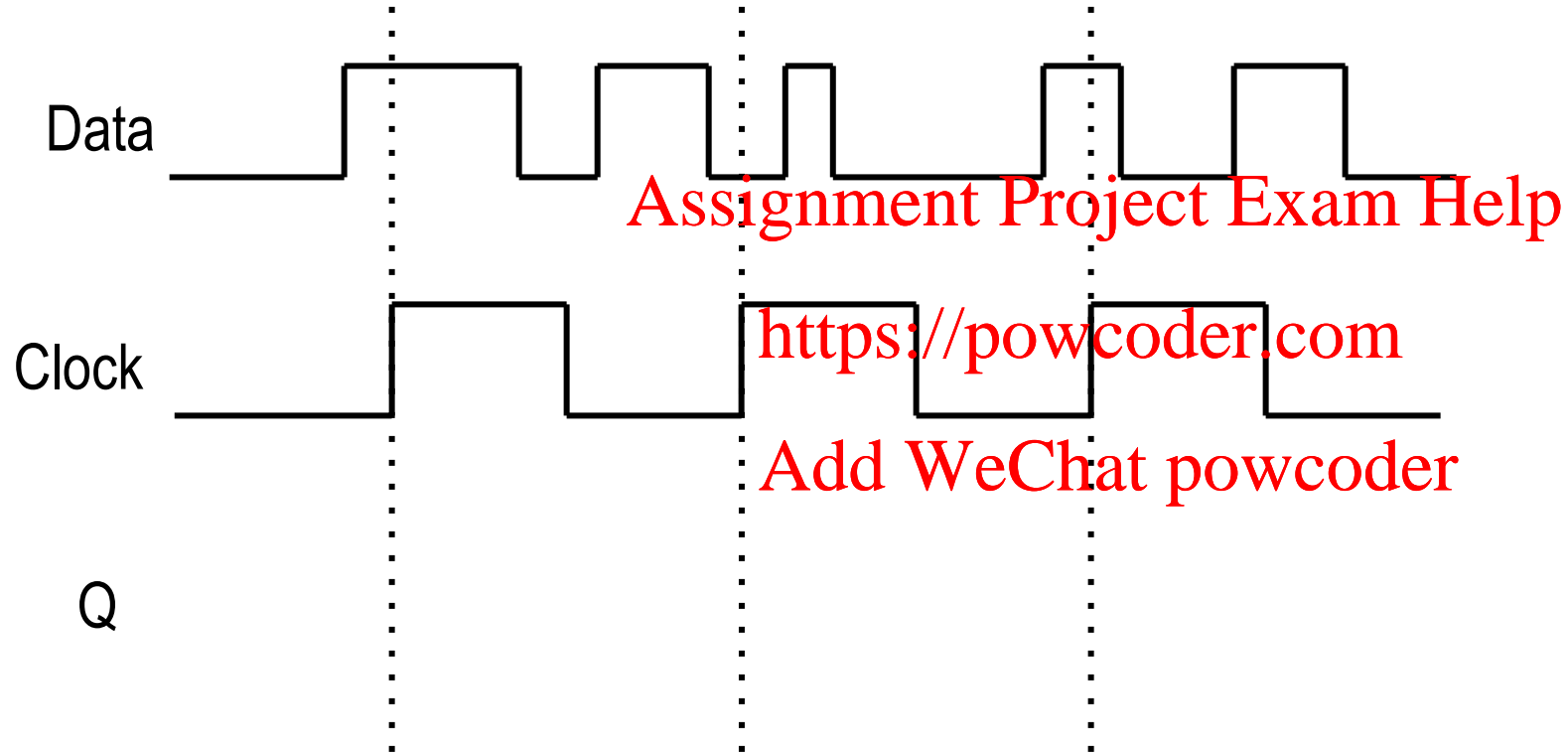

What Happens if Data Changes on a Clock Edge?


Sequential
Logic

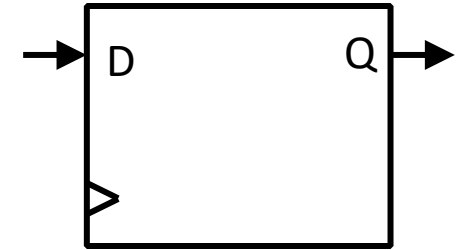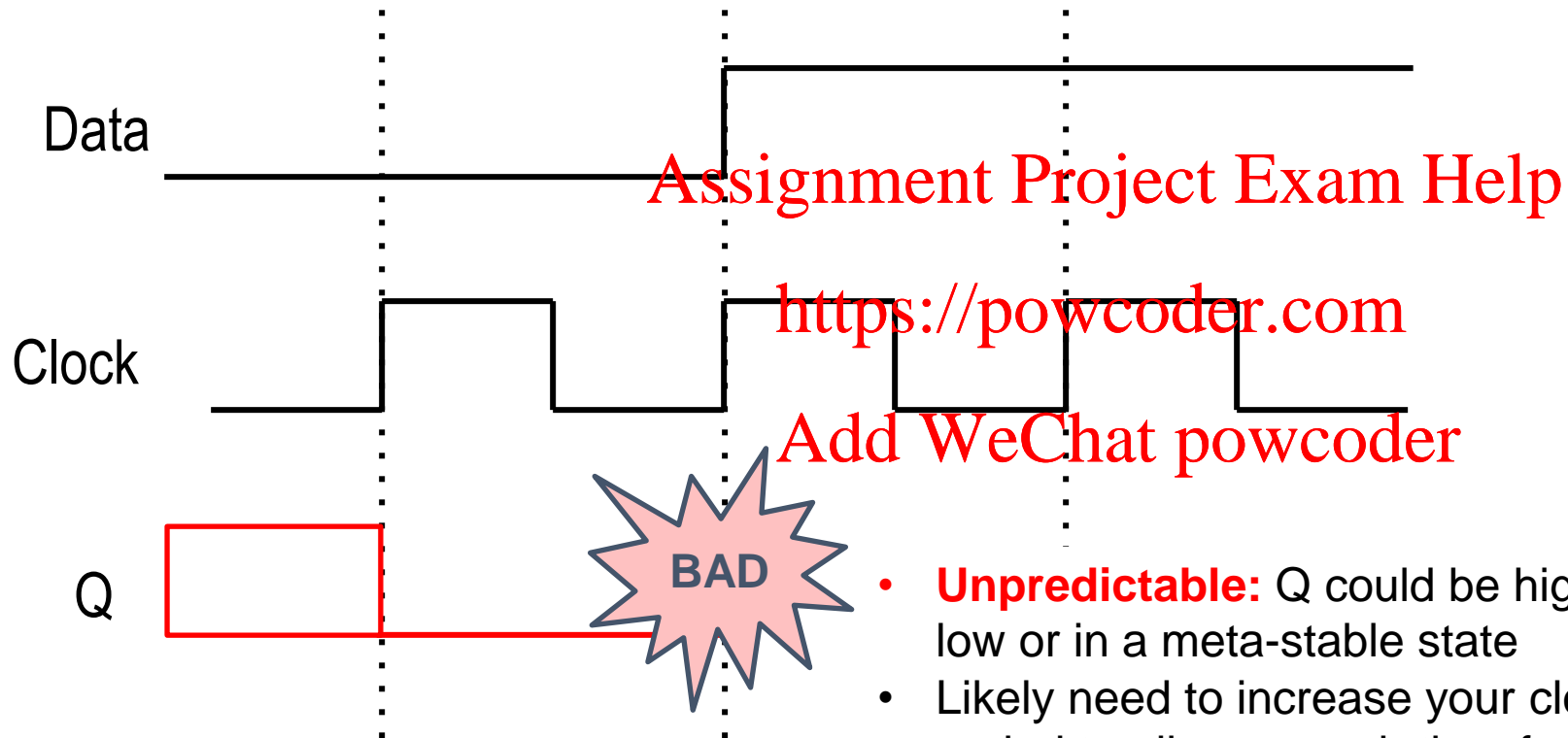

- **Unpredictable:** Q could be high, low or in a meta-stable state
- Likely need to increase your clock period to allow enough time for signal propagation


Why Edge-Triggered Flip-Flops?

Latch

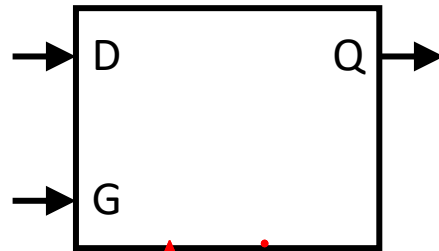

Assignment Project Exam Help

Flip-flop

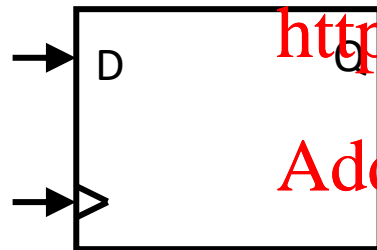

<https://powcoder.com>

Add WeChat powcoder


In edge-triggered flip-flops, the latching edge provides convenient abstraction of “instantaneous” change of state.

Adding an Enable Input

- Q only updates on a positive clock edge if 'en' is high
- Think of 'en' as 'write enabled'

Assignment Project Exam Help

<https://powcoder.com>

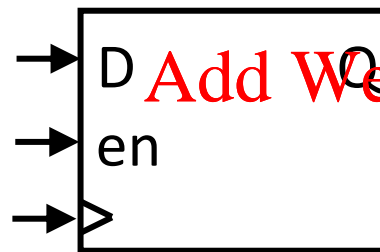

Add WeChat powcoder

Logistics

- There are 3 videos for lecture 9
 - L9_1 – Combinational-Logic-Timing
 - L9_2 – Memory_Latches-Clocks
 - L9_3 – Finite-State-Machines
- There are two worksheet for lecture 9
 1. Circuit design – combinational logic
 2. Circuit design – sequential logic – you are ready for this now

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



L9_3 Finite-State-Machines

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder

Learning Objectives

- To define and understand the concept of state as it pertains to architecture
- Ability to model a controller as a machine expressed as states and transitions, i.e., a finite state machine.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Finite State Machines

- So far we can do two things with gates:
 1. Combinational Logic: implement Boolean expressions
 - Adder, MUX, Decoder, logical operations etc
 2. Sequential Logic: store state
 - Latch, Flip-Flops
- How do we combine them to do something interesting?
 - Let's take a look at implementing the logic needed for a vending machine
 - Discrete states needed: remember how much money was input
 - Store sequentially
 - Transitions between states: money inserted, drink selected, etc
 - Calculate combinational or with a control ROM (more on this later)

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

State

Very important concept in architecture

- Represents all the stored information in a system at a point in time
- Finite State Machine:
 - Model of a system which enumerates all states that system may be in, and the conditions which allow transitions between states
 - Often expressed as a directed graph or table

FSM Example – Vending Machine

- We could use a general purpose processor
- However, a custom controller will be:
 - Faster
 - Lower power
 - Cheaper to produce in high volume
- On the other hand, a custom controller:
 - Will be slower to design
 - More expensive in low volume
- Goals:
 - Take money, vend drinks.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Input and Output

- Inputs:

- Coin trigger
- Refund button
- 10 drink selectors
- 10 pressure sensors
 - Detect if there are still drinks left

- Outputs:

- 10 drink release latches
- Coin refund latch



Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Operation of Machine

- Accepts quarters only
- All drinks are \$0.75
- Once we get the money, a drink can be selected
- If they want a refund, release any coins inserted
- No free drinks!
- No stealing money.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Building the Controller

- Finite State
 - Remember how many coins have been put in the machine and what inputs are acceptable
- Read-Only Memory (ROM)
 - Define the outputs and state transitions
- Custom combinational circuits
 - Reduce the size (and therefore cost) of the controller

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

Finite State Machines

A Finite State Machine (FSM) consists of:

- K states: $S = \{s_1, s_2, \dots, s_k\}$, s_1 is initial state
- N inputs: $I = \{i_1, i_2, \dots, i_n\}$
- M outputs: $O = \{o_1, o_2, \dots, o_m\}$
- Transition function $T(S, I)$ mapping each current state and input to next state
- Output Function $P(S)$ or $P(S, I)$ specifies output
 - $P(S)$ is a Moore Machine
 - $P(S, I)$ is a Mealy Machine

FSM for Vending Machine

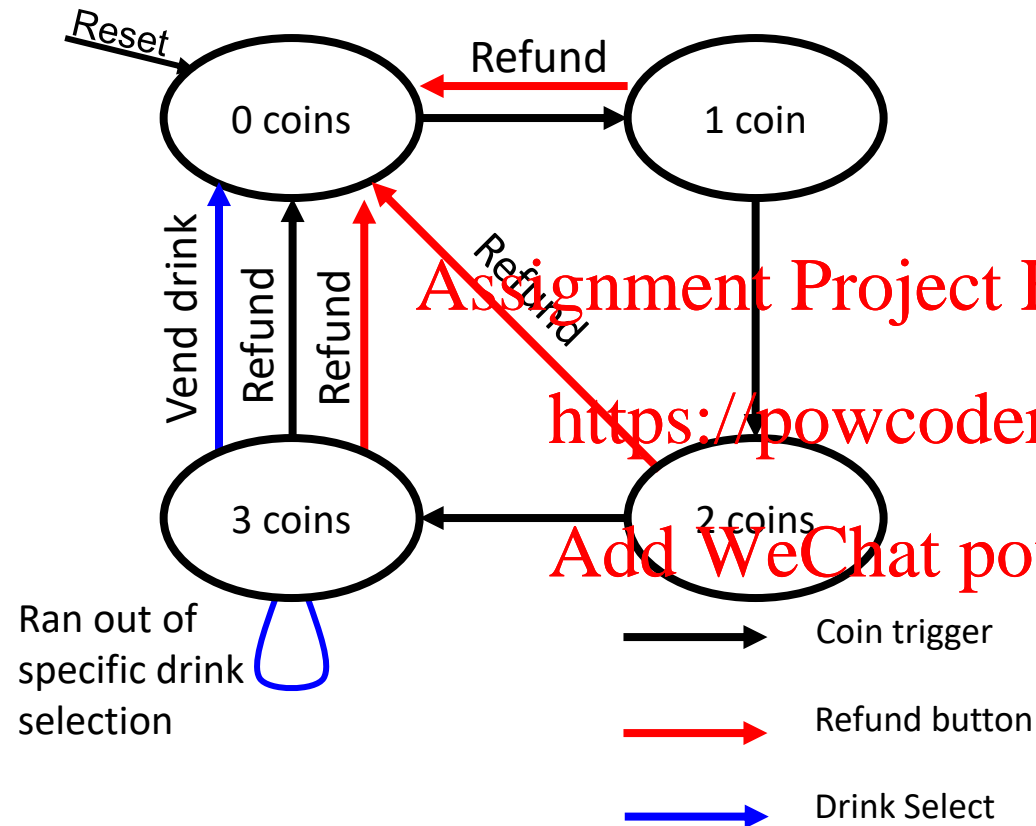


Ran out of specific drink selection

Is this a Mealy or Moore Machine?

Mealy ~ output is based on current state
AND input



Implementing a FSM

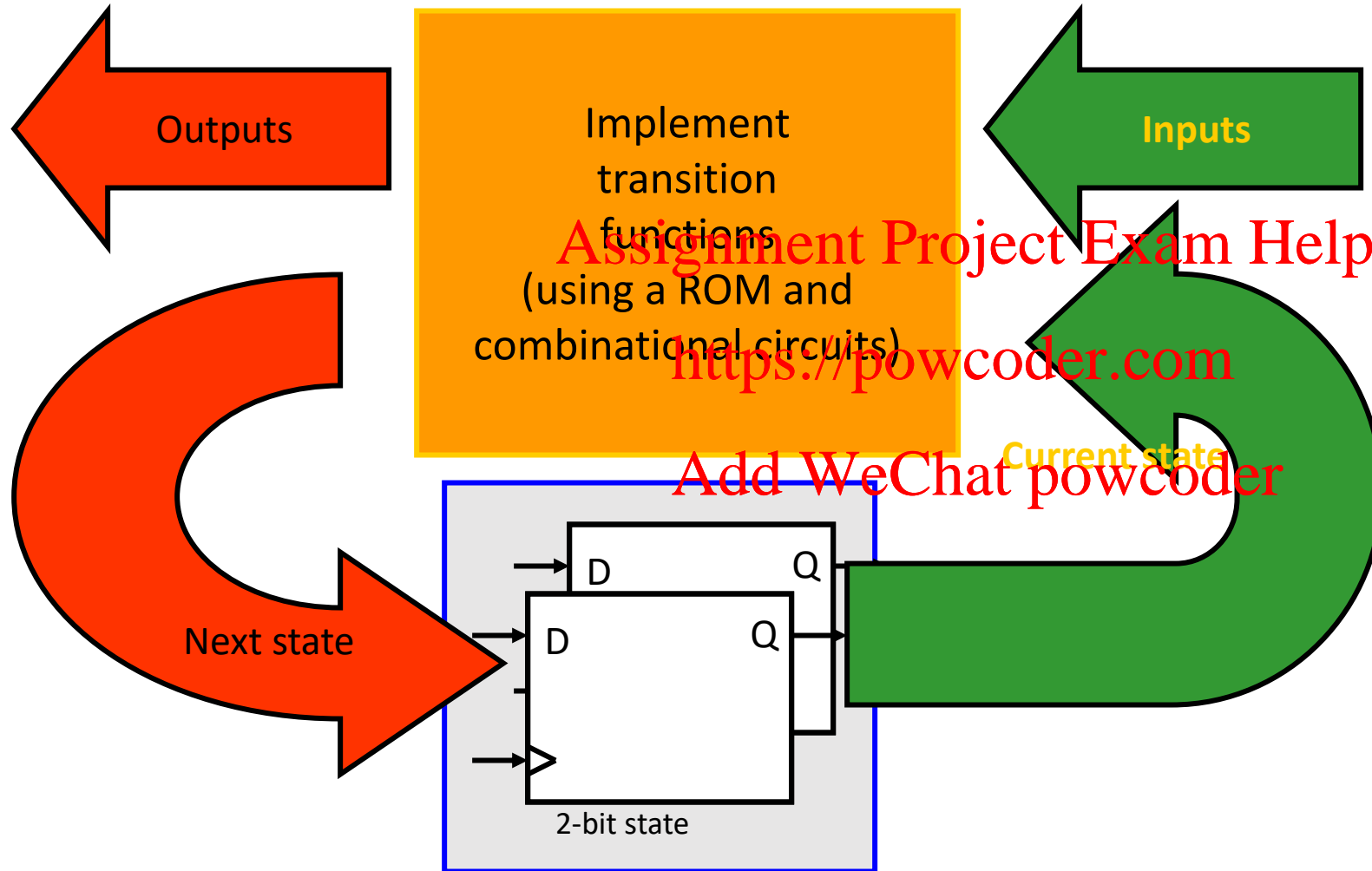

Logistics

- There are 3 videos for lecture 9
 - L9_1 – Combinational-Logic-Timing
 - L9_2 – Memory_Latches-Clocks
 - L9_3 – Finite-State-Machines
- There are two worksheet for lecture 9
 1. Circuit design – combinational logic
 2. Circuit design – sequential logic

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder