

L8_1 Floating-Point Arithmetic

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder



Learning Objectives

- To understand the algorithm for arithmetic operations using IEEE 754 floating-point values.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Floating Point Representation

$$10.625_{10} \rightarrow 1010.101_2$$


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

$$1.010101 \times 2^3$$

This must be a 1!
So don't store it.

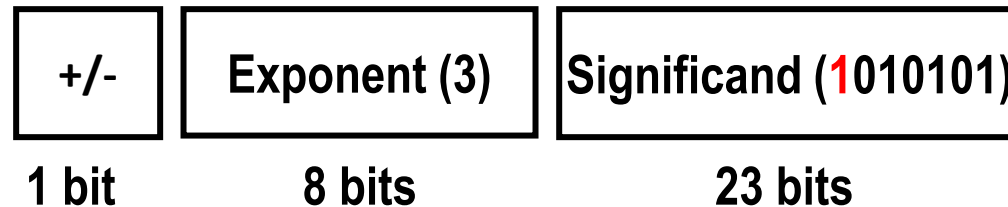

$$10.625_{10} = 0 \quad 10000010 \quad 01010100000000000000000_2$$

Floating Point - Example

Problem: What is the value (in decimal) of the following IEEE 754 floating point encoded number?

1	10000101	010110010000000000000000
---	----------	--------------------------

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

sign bit	1	- (negative)
----------	---	--------------

exponent	10000101	$133 - 127 = 6$ (biased by 127)
----------	----------	---------------------------------

significand	010110010000000000000000	add implicit 1
-------------	--------------------------	----------------

-1.01011001×2^6	shift radix point 6 places	-1010110.01
--------------------------	----------------------------	---------------

$$-1010110.01 = -(2^6 + 2^4 + 2^2 + 2^1 + 2^{-2}) = -(64 + 16 + 4 + 2 + \frac{1}{2}) = -86.25_{10}$$

Floating Point Multiply - Example

10.625 ₁₀

10 ₁₀

Algorithm:

1. Convert to binary
2. Convert binary numbers to IEEE 754 floating-point
3. Multiply
 1. Sign bit - xor
 2. Add exponents - *mind the bias! (127)*
 3. Multiply significands

Floating Point Multiply - Example

$10.625_{10} = 1010.101_2$ \Rightarrow

0	10000010	010101000000000000000000
0	10000010	010000000000000000000000
		×
		101010010000000000000000

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

$$\begin{array}{r}
 1010101 \\
 \times 101 \\
 \hline
 1010101 \\
 0000000 \\
 1010101 \\
 \hline
 110101001
 \end{array}$$

1101010.01_2
 $= 106.25_{10}$

Floating Point Addition

- More complicated than floating point multiplication!
- If exponents are unequal, must shift the significand of the smaller number to the right to align the corresponding place values
- Once numbers are aligned, simple addition (could be subtraction, if one of the numbers is negative)
- Renormalize (shift to get back into proper "scientific notation")
- Added complication: rounding to the correct number of bits to store could denormalize the number, and require one more step

Floating Point Addition

1. Shift smaller exponent right to match larger.
2. Add significands
3. Normalize and update exponent
4. Check for "out of range"


Normalize: shift significand (mantissa) for integer part to be 1 and remaining bits are fractions

Example:
 1010.101_2
Normalized is
 1.010101×2^3

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

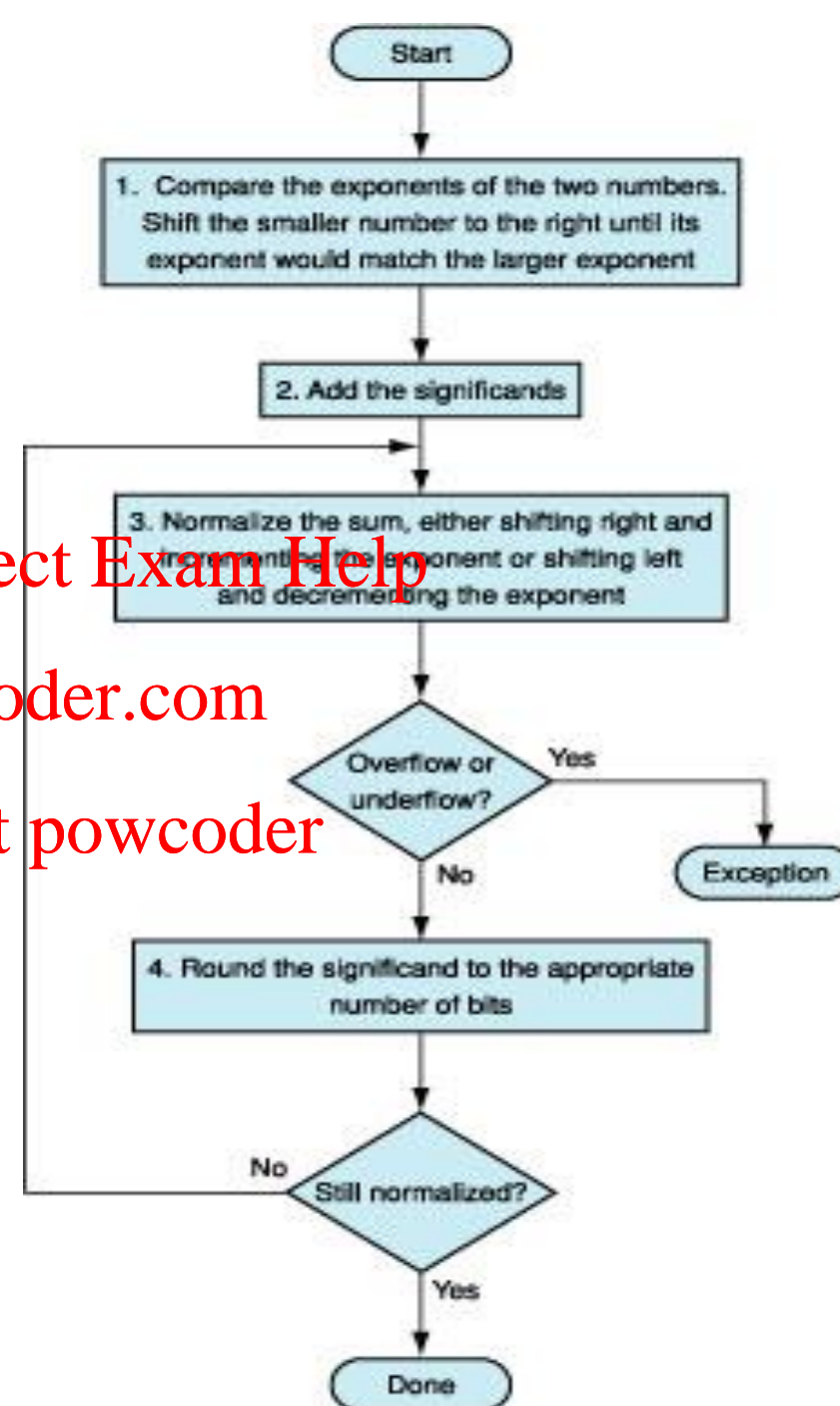

Floating
Point

Floating Point Addition - Example

Problem: Add two numbers using IEEE floating point addition: **101.125 + 13.75**

1. Convert to IEEE 754 format
2. Shift smaller exponent right to match larger.
3. Add significands
4. Normalize and update exponent
5. Check for "out of range"

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Floating Point Addition - Example

Problem: Add two numbers using IEEE floating point addition: **101.125 + 13.75**

~~Assignment Project Exam Help~~

~~<https://powcoder.com>~~

~~Add WeChat powcoder~~

Shift mantissa by difference in exponent

Shift by 6 - 3 = 3

101.125 0 10000101 100101001000000000000000

13.75 0 10000010 101110000000000000000000

13.75 0 10000101 001101110000000000000000

0 10000101 110010111000000000000000

$$= 1.110010111_2 \times 2^6 = 114.875_{10}$$

Sum Significands

```


  1 1 0 0 1 0 1 0 0 1
+ 0 0 0 1 1 0 1 1 1 0
-----
  1 1 1 0 0 1 0 1 1 1
  
```

Sum didn't overflow, so no re-normalization needed

More Precision and Range

- We have described IEEE-754 binary32 floating point format, commonly known as “single precision” (“float” in C/C++)
 - 24 bits precision; equivalent to about 7 decimal digits
 - $3.4 * 10^{38}$ maximum value
 - Good enough for many but not all calculations
- IEEE-754 also defines a larger binary64 format, “double precision” (double data type in C/C++)
 - 53 bits precision, equivalent to about 16 decimal digits
 - $1.8 * 10^{308}$ maximum value
 - Most accurate physical values currently known only to about 47 bits precision, about 14 decimal digits

Floating Point Precision

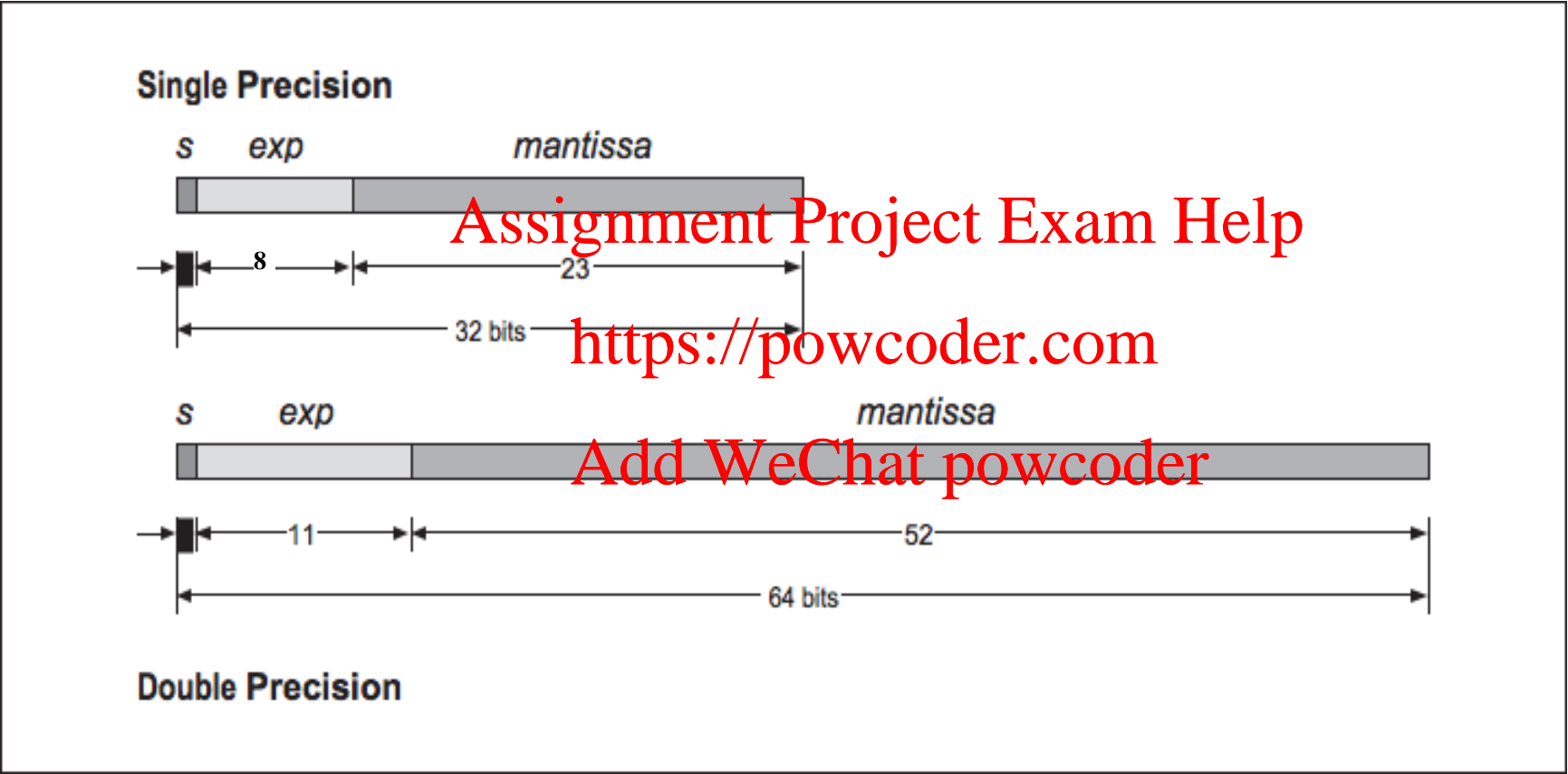

Assignment Project Exam Help
<https://powcoder.com>
 Add WeChat powcoder


Logistics

- There are 3 videos for lecture 8
 - L8_1 – IEEE_Floating-Point_Arithmetic
 - L8_2 – Basic-Electronics-Logic_Gates
 - L8_3 – Combinational-Logic
- There is one worksheet for lecture 8
 1. Logic gates – complete at the end of all 3 videos.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



L8_2 Basic-Electronics_Logic-Gates

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder

Office Hours

- Drop by office hours, ask questions, say 'hi'
- Just in case you did not see them on the calendar:
Tuesdays 11am to 12 noon (EST) – individual meetings

Assignment Project Exam Help

<https://powcoder.com>

Group office hours Add WeChat powcoder

Tuesdays 4pm to 4:30 pm

Thursdays 9:45 am to 10:15 am

Thursdays 2:30 pm to 3:00 pm

<https://umich.zoom.us/j/92153246345>

Learning Objectives

- To identify logic gates used in combinational logic circuits and describe their operations.
- Be able to create the functionality of any logic gate with the NOR gate, (and therefore, the nor instruction in LC-2K).

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Levels of Abstraction

- Quantum level, solid state physics
- Conductors, Insulators, Semiconductors
- Doping silicon to make diodes and transistors
- Simple gates, Boolean logic, and truth tables
- Combinational logic: muxes, decoders
- Clocks
- Sequential logic: latches, memory
- State machines
- Processor Control: Machine instructions
- Computer Architecture: Defining a set of instructions

Assignment Project Existence Help

<https://powcoder.com>

Add WeChat powcoder

Start with the Materials: Conductors and Insulators

- **Conductor**: a material that permits electrical current to flow easily. (low resistance to current flow)
 - Lattice of atoms with free electrons
- **Insulator**: a material that is a poor conductor of electrical current (High resistance to current flow)
 - Lattice of atoms with strongly held electrons
- **Semi-conductor**: a material that can switch between an (okay) conductor and an (okay) insulator
 - Controlled via an external voltage
 - Basis for "logical switches" that make up digital circuits


Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

Making a Transistor

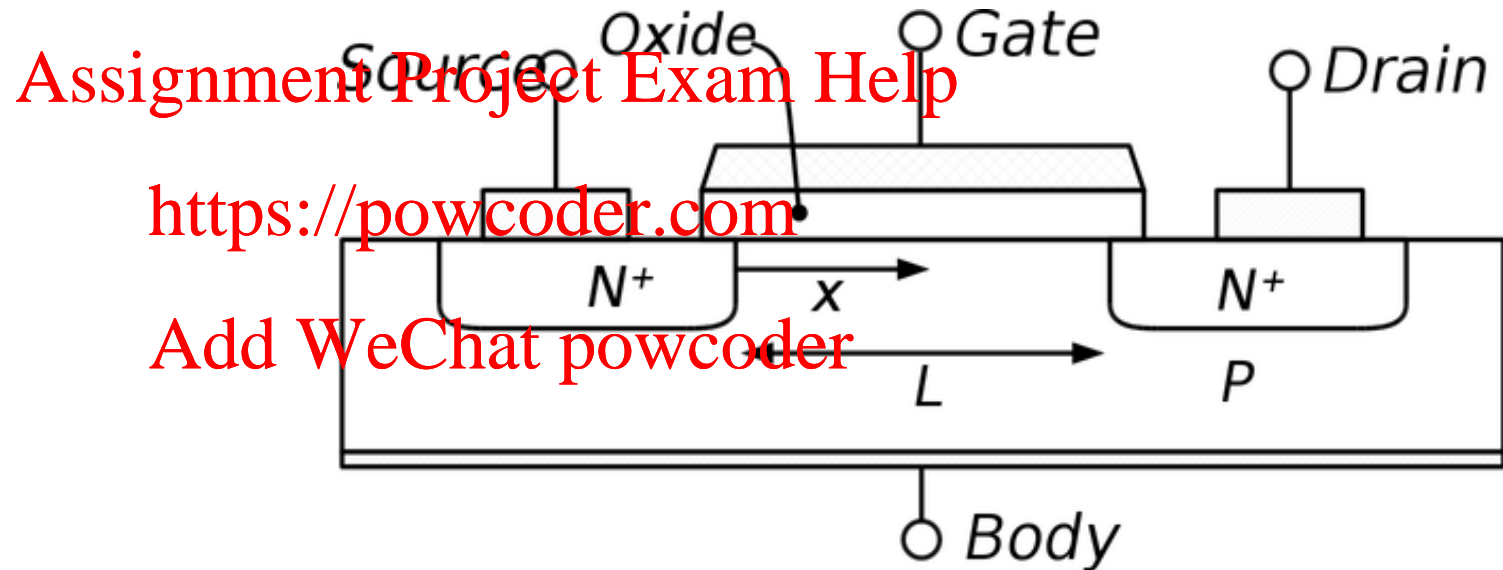- Our first level of abstraction is the transistor (basically 2 diodes sitting back-to-back)




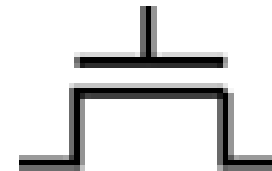- Electrical engineers use a symbol like this:




Recent Pictures and the Near Future

Source: Intel

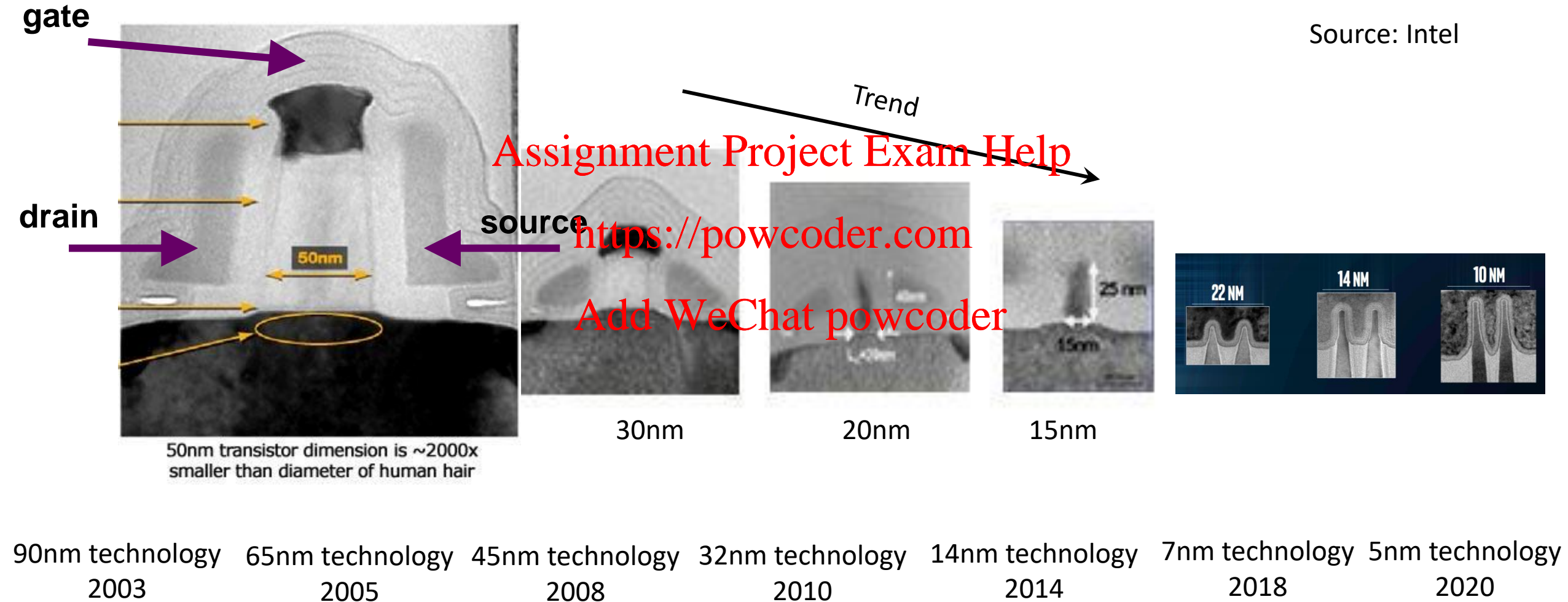


Transistor Count

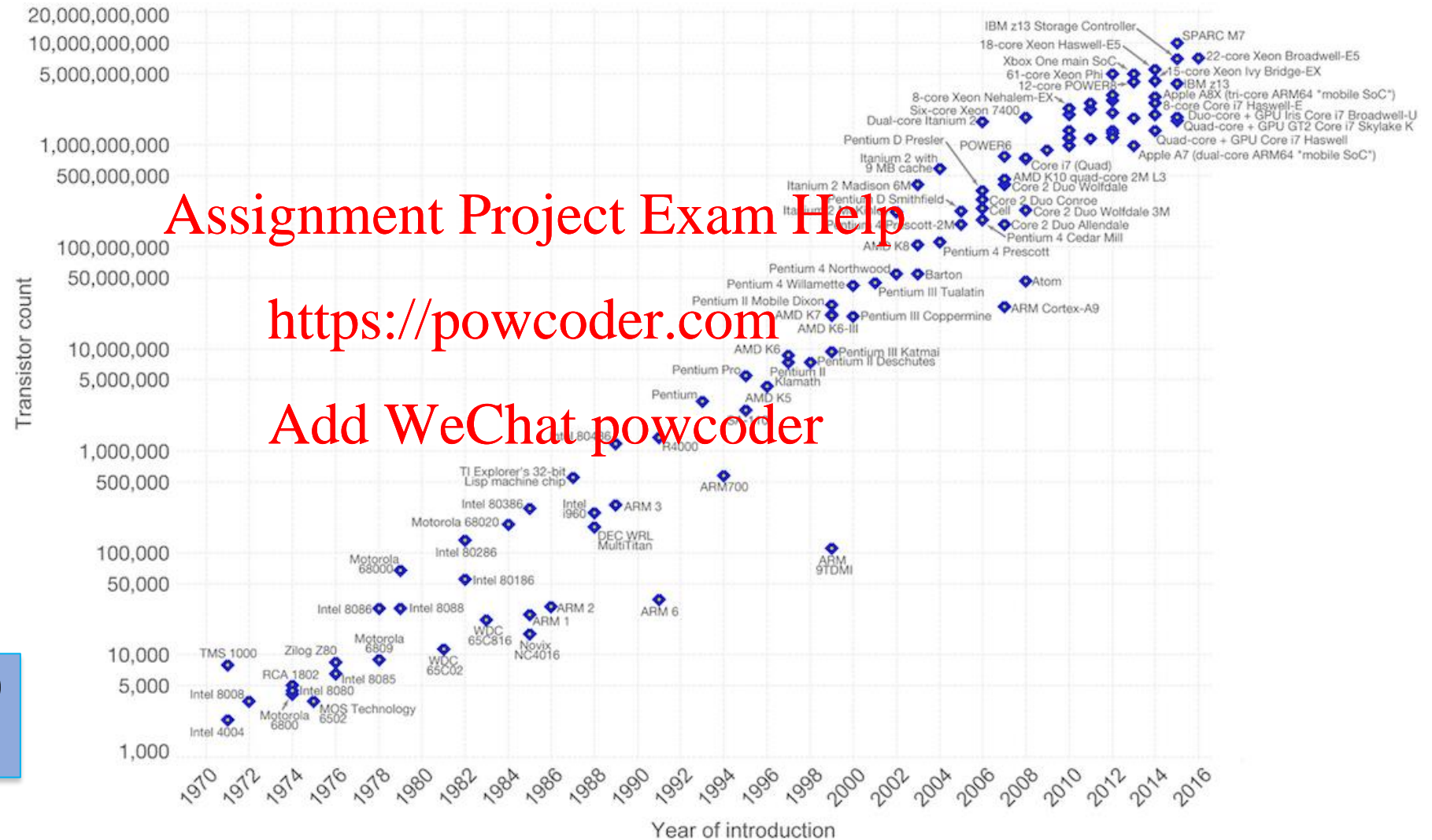

2020 - NVIDIA RTX 3090
28 Billion Transistors

Present and Future Problems

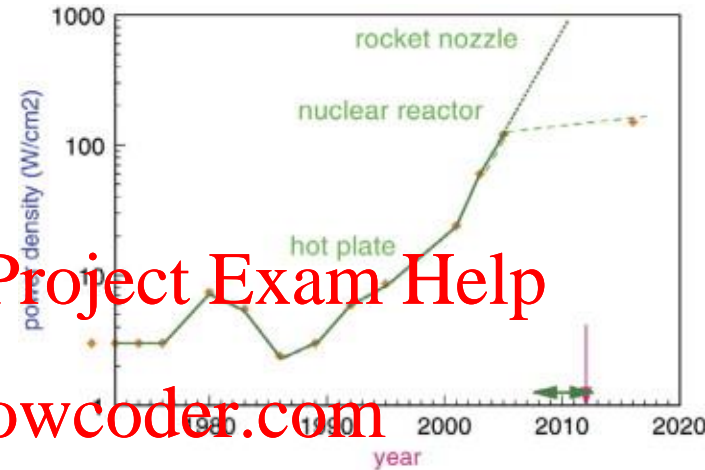
- Area is the least of them
- Power density – Watts/mm²
- Leakage current





Assignment Project Exam Help

<https://powcoder.com>

- Reliability (faults)

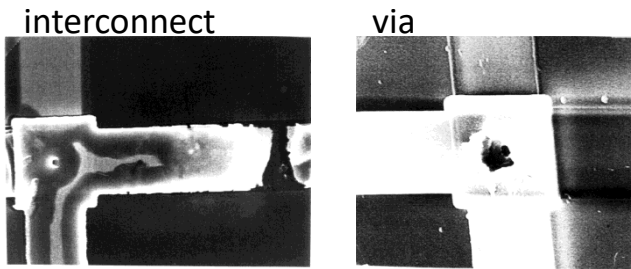


Add WeChat powcoder

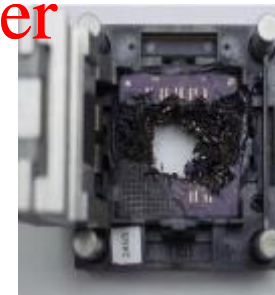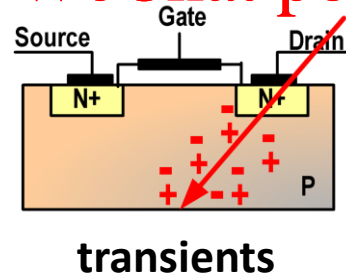

Testing burn-in

- Process variation (not all transistors are equal)

As for power: Cooking-aware Computing

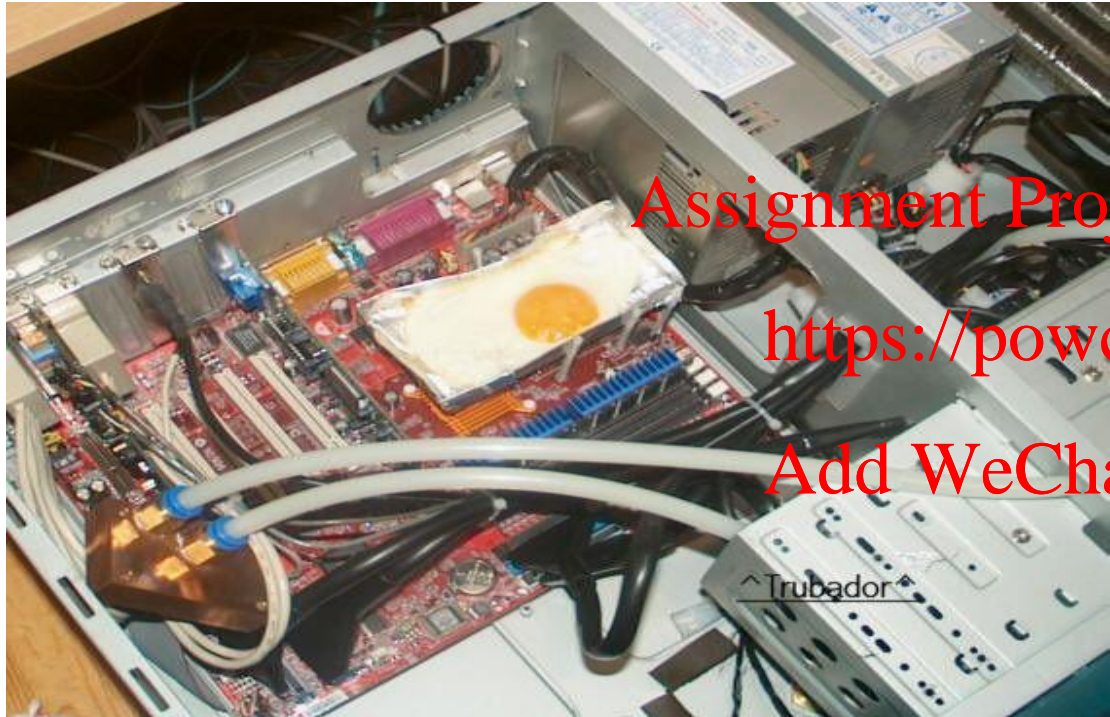

Source: The New York Times, 25 June 2002



Liquid Nitrogen Cooling


Basic Gate: Inverter

CS abstraction
- logic function

Truth Table

I	O
0	1
1	0

Schematic symbol (CS/EE)

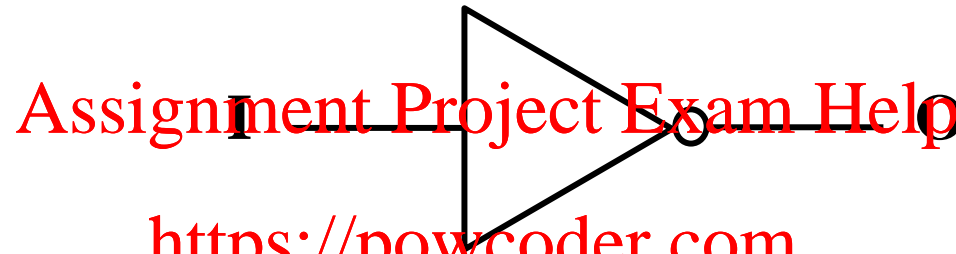

<https://powcoder.com>

Add WeChat powcoder

Basic Gate: NAND

Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder



Basic Gates: AND, OR, XOR


AND

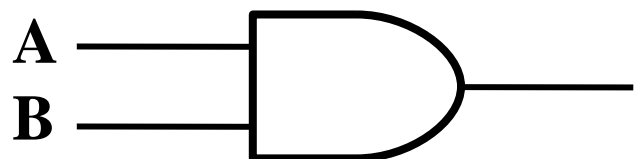

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


OR

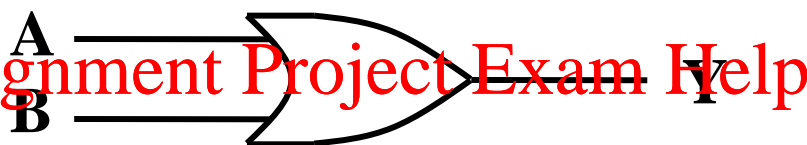

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

XOR

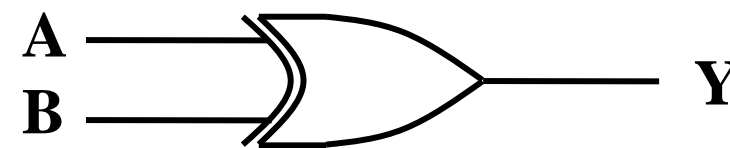

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Basic Gates: NOR

NOR

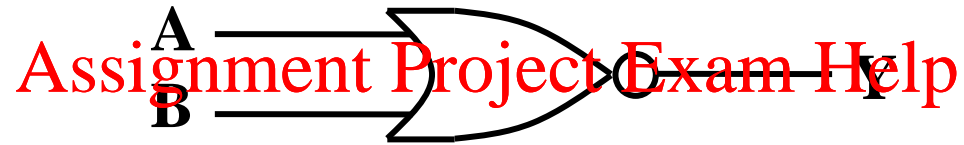

<https://powcoder.com>

Truth Table

Add WeChat powcoder

A	B	$A \mid B$	Y
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Logic Gate Exercise

- NOR is logically complete
 - This means that all gates can be implemented using only NORs
 - All gates can be implemented in LC2K
 - NAND is also logically complete
- Exercise:
 - Implement INV using only NOR gates
 - Implement AND using only NOR gates
 - Implement OR using only NOR gates
 - Hint Demorgan's Law:
 - $A \mid\mid B = \neg(\neg A \ \&\& \ \neg B)$
 - $\neg(A \mid\mid B) = \neg A \ \&\& \ \neg B$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Logic Gate Exercise – INV (!) using NOR

$!(A \ || \ B) = A \ \text{NOR} \ B$
 substitute A for B
 $!(A \ || \ A) = A \ \text{NOR} \ A$
 $!(A) = A \ \text{NOR} \ A$
 $!A = A \ \text{NOR} \ A$

NOR





Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

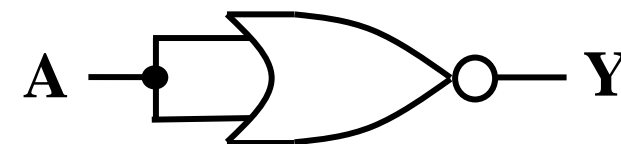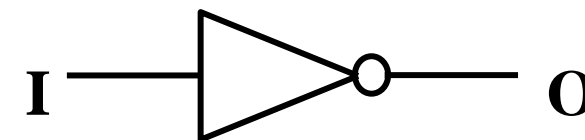

Truth Table

I	O
0	1
1	0

Logic Gate Exercise – AND using NOR

$$\neg(A \vee B) = \neg A \wedge \neg B = A \text{ NOR } B$$

$$\neg A \text{ NOR } \neg B = A \wedge B$$

substitute A NOR A for !A


substitute B NOR B for !B

$$A \wedge B = (A \text{ NOR } A) \text{ NOR } (B \text{ NOR } B)$$

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

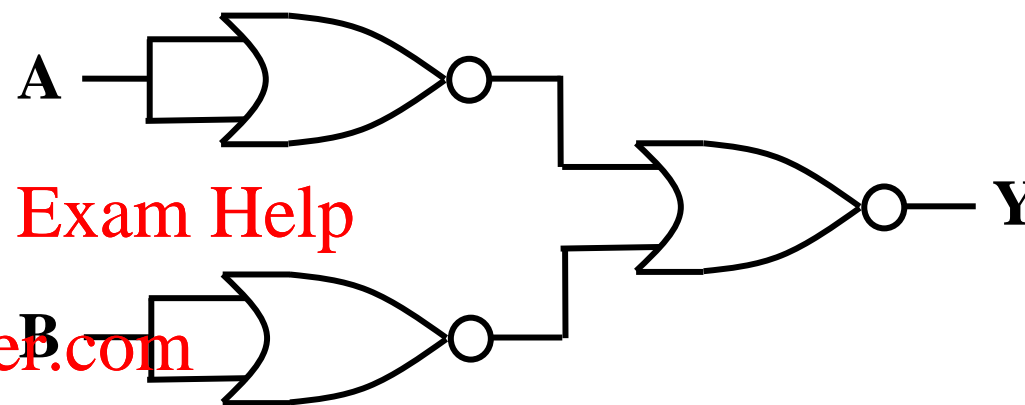


A	B	A && B	Y
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

Logic Gate Exercise – OR using NOR

NOR

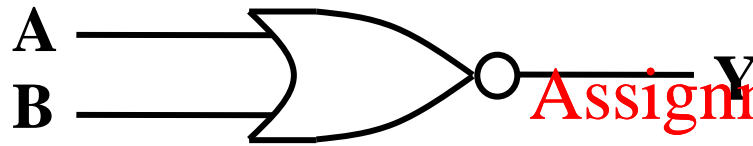

OR

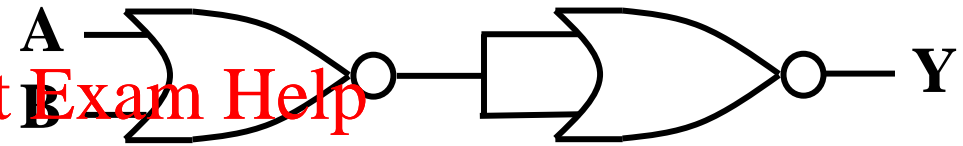

Assignment Project Exam Help

<https://powcoder.com>

Truth Table

Add WeChat powcoder

A	B	$A \mid B$	Y	$\neg Y$
0	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	0	1

Logistics

- There are 3 videos for lecture 8
 - L8_1 – IEEE_Floating-Point_Arithmetic
 - L8_2 – Basic-Electronics-Logic_Gates
 - L8_3 – Combinational-Logic
- There is one worksheet for lecture 8
 1. Logic gates – complete at the end of all 3 videos.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



L8_3 Combinational-Logic

Assignment Project Exam Help

<https://powcoder.com>

EECS 370 – Introduction to Computer Organization – Fall 2020

Add WeChat powcoder



Learning Objectives

- To create circuits using combinations of basic gates.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Building Complexity: Addition (1)

GOAL: We want to design a circuit that performs binary addition


Let us start by adding two bits

- Design a circuit that takes two bits as input (A and B)
- Generates a sum and carry bit (S and C)

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

	0	1	1	0
	1	0	1	1
+	0	0	1	1
	1	1	1	0
	1	1	1	0
	1	1	1	0

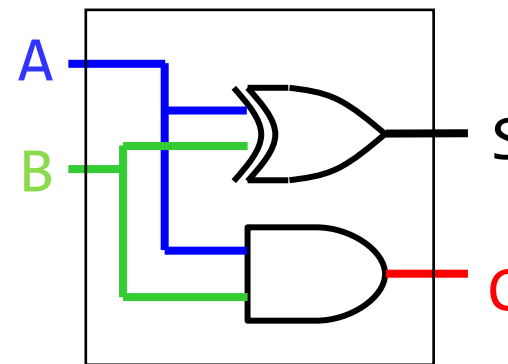1. Make a truth table
2. Design a circuit



Half-Adder

Building Complexity: Addition (1)


$$\begin{array}{r}
 0\ 1\ 1\ 0 \\
 1\ 0\ 0\ 1\ 1 \\
 +\ 0\ 0\ 1\ 1\ 0 \\
 \hline
 1\ 1\ 0\ 0\ 1
 \end{array}$$

- Now we can add two bits, but how do we deal with carry bits?
 - We must design a circuit that can add three bits
 - Inputs: A, B, Cin
 - Outputs: S, Cout
- 1. Design a truth table
- 2. Circuit
- How do we combine these?

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

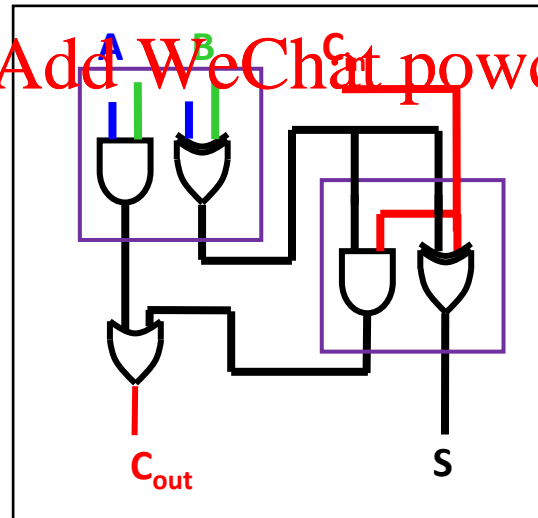

Cin	A	B	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

8-bit Ripple Carry Adder

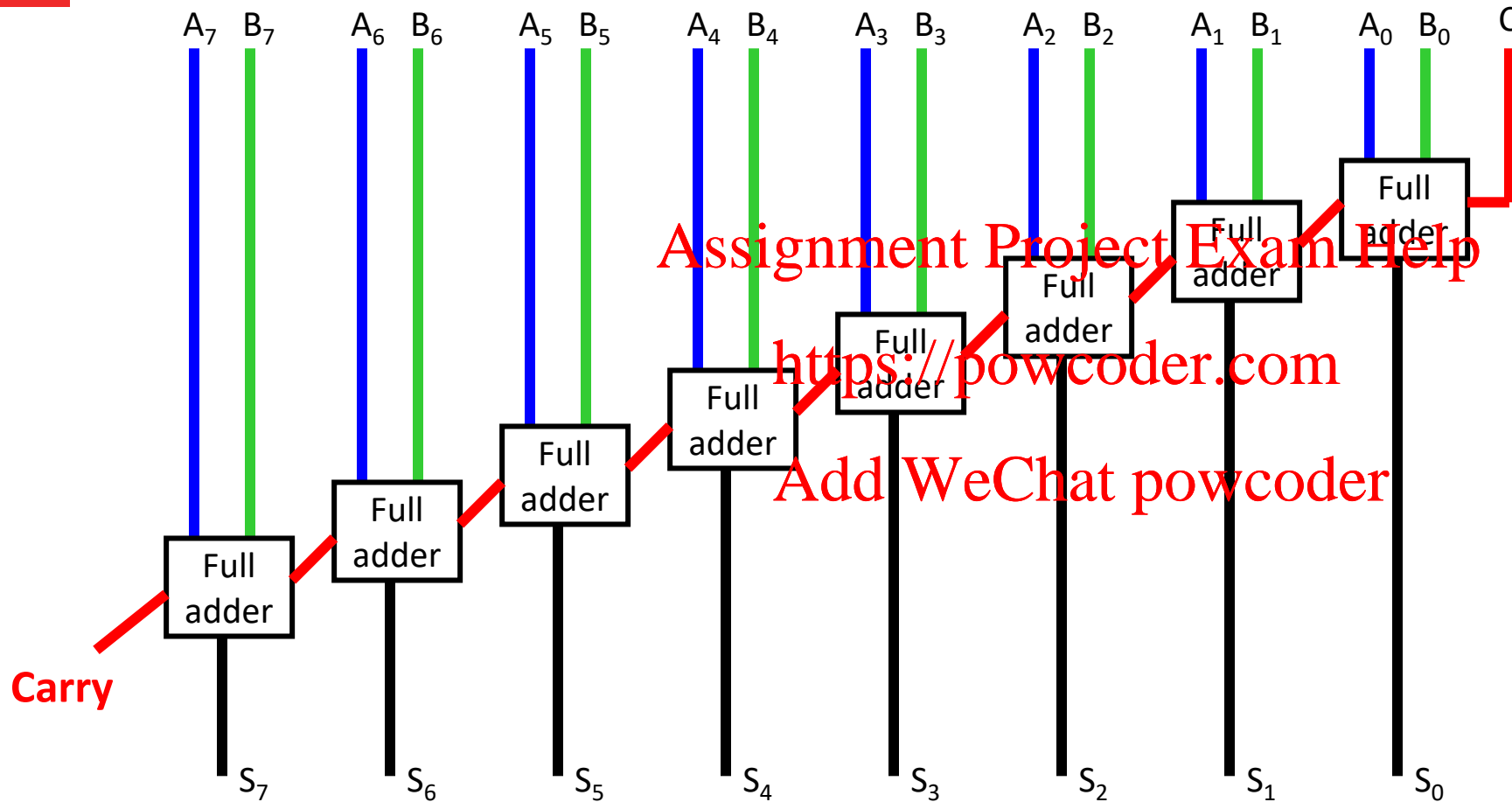

Unfortunately, this has a very large propagation time for 32 or 64 bit adds

Building Complexity: Selecting

- We want to design a circuit that can select between two inputs - Let us start with a one-bit version



A	B	S	C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Draw a truth table

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

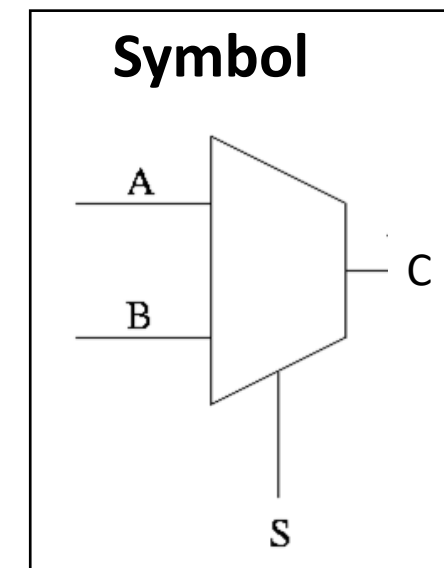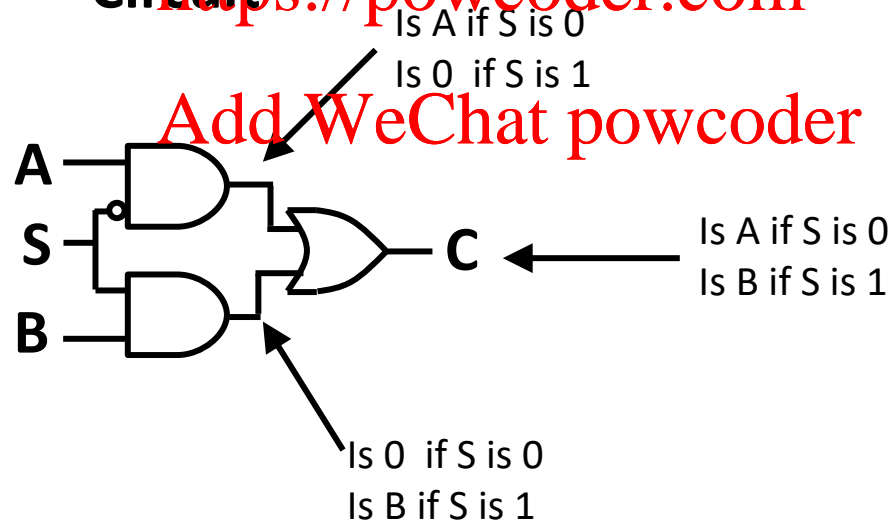

Multiplexer (Mux)

Comb. Logic


Multiplexer - Example

Problem: Build a 4x1 mux using only 2x1 muxes

Assignment Project Exam Help



<https://powcoder.com>

Add WeChat powcoder

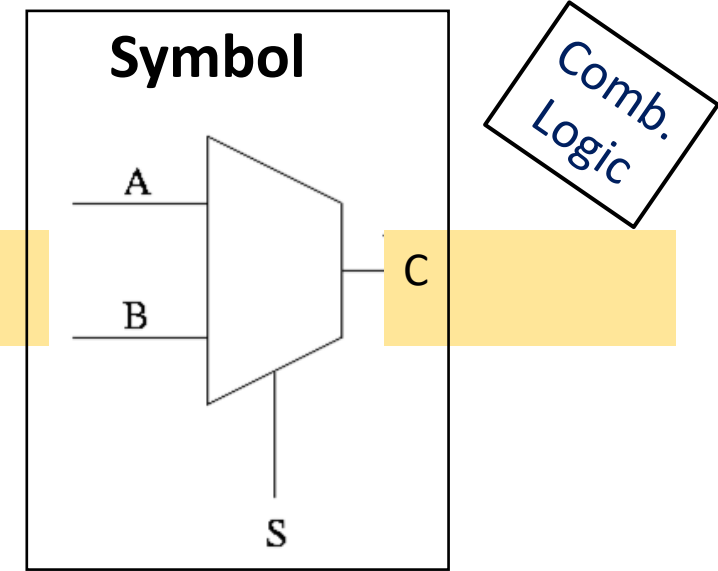

Multiplexer - Example

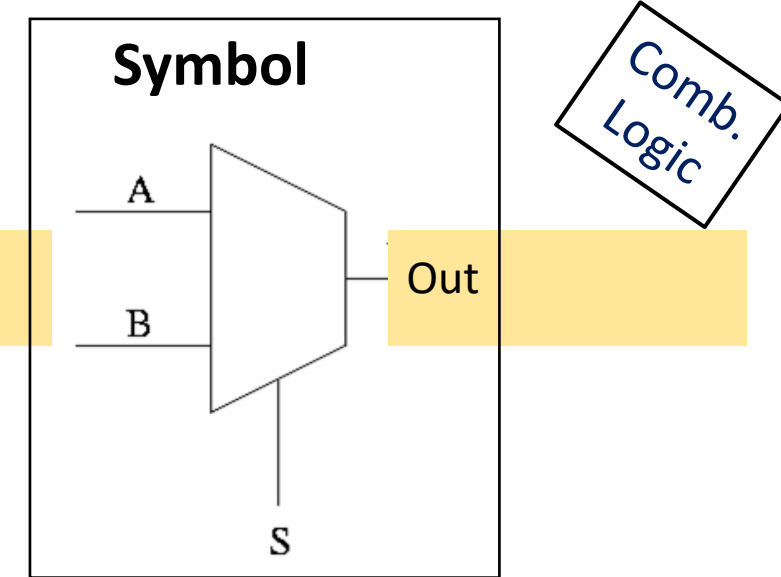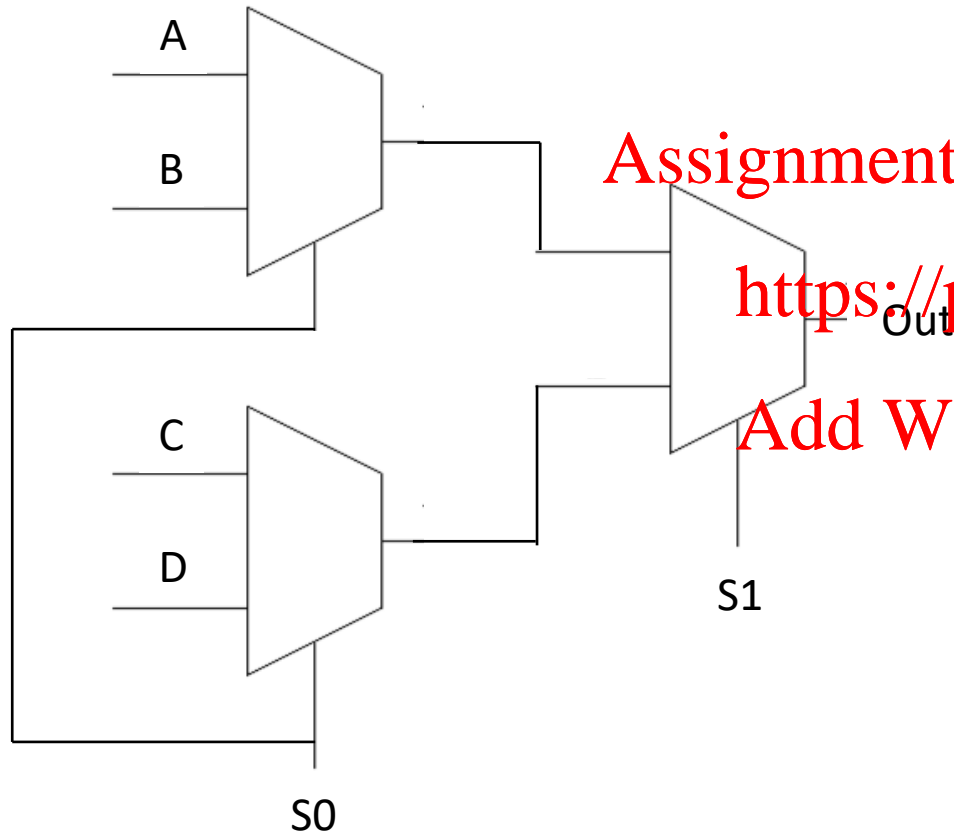Problem: Build a 4x1 mux using only 2x1 muxes



Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

S1	S0	Out
0	0	A
0	1	B
1	0	C
1	1	D


Building Complexity: Decoding

- Another common device is a decoder
 - Input: N-bit binary number
 - Output: 2^N bits, exactly one of which will be high

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

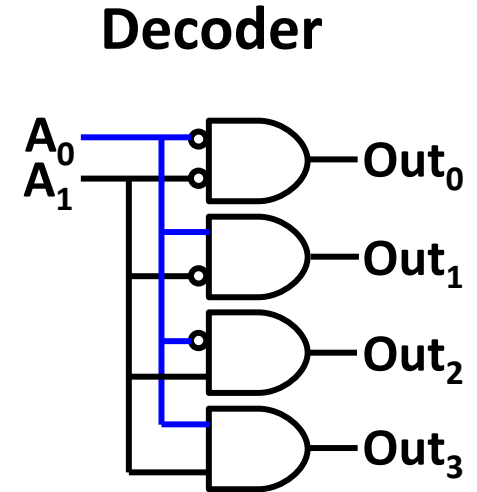

Combinational Circuits Implement Boolean Expressions


- Output is determined exclusively by the input
- No memory: Output is valid only as long as input is
 - Adder is the basic gate of the ALU (Future lecture)
 - Decoder is the basic gate of indexing
 - MUX is the basic gate controlling data movement

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder


Half-Adder

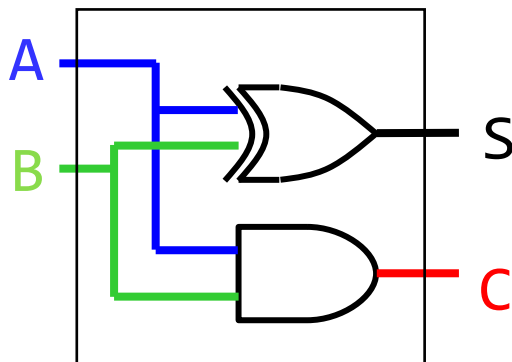

Decoder

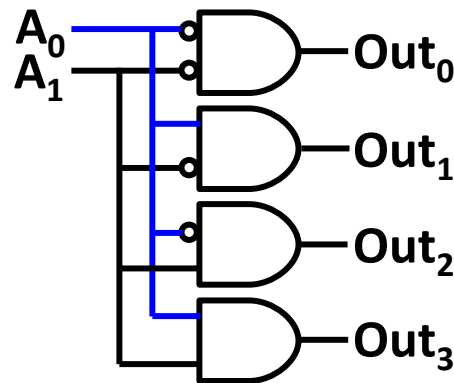

Mux

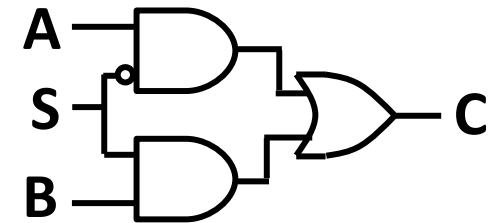

Logistics

- There are 3 videos for lecture 8
 - L8_1 – IEEE_Floating-Point_Arithmetic
 - L8_2 – Basic-Electronics-Logic_Gates
 - L8_3 – Combinational-Logic
- There is one worksheet for lecture 8
 1. Logic gates – complete at the end of all 3 videos.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder